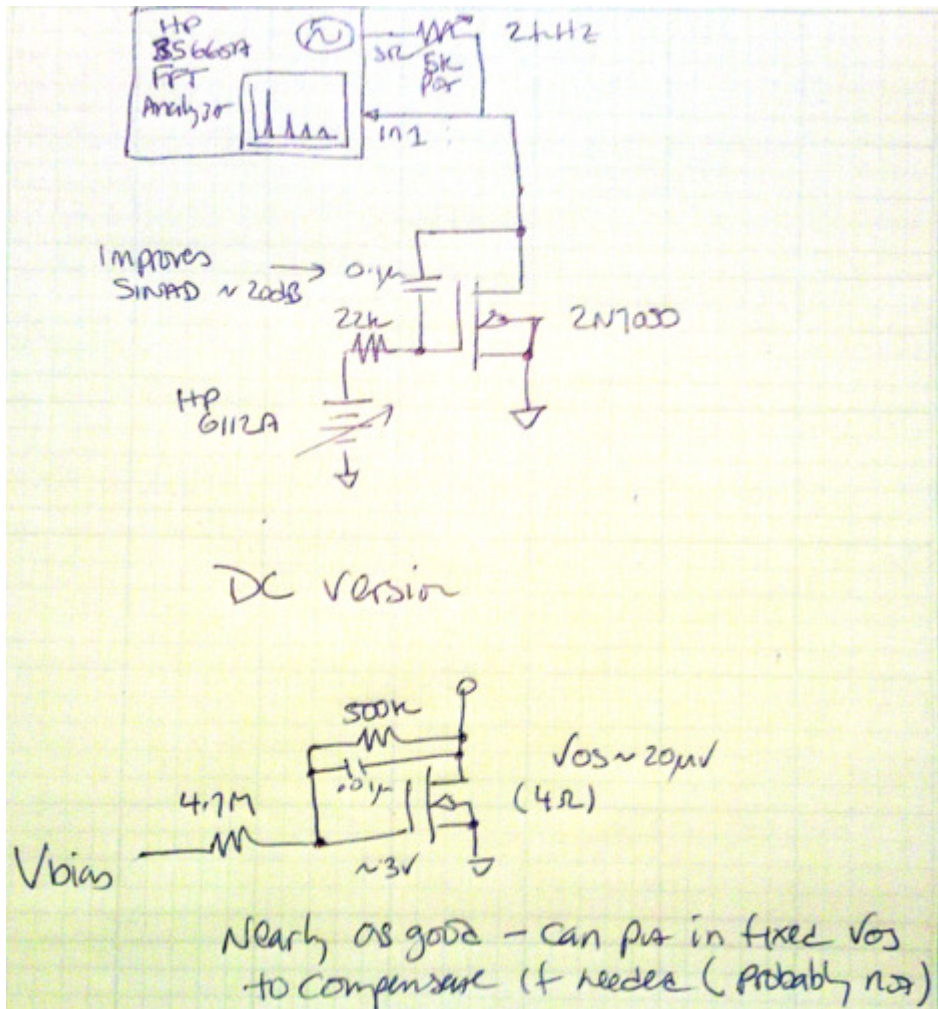


2N7000 Variable Resistor

Phil Hobbs 9/23/09

Setup: HP 35665A source (5 Vpk) -> 1k / 5k resistor -> 2N7000 D-S


Source resistor 22k, 0.1 uF G->D bypass! (1:1 NOT 1:2 ratio)-> 16 dB THD reduction



imax := 20		i := 0..imax - 1		Vgs_i := 2.0 + i*0.1		mV := 0.001		Vgs_i =																	
R :=	(36.17	V _{5mA} :=	(155.2	·mV THD% _{5mA} :=	(5.2	<table border="1"> <tr><td>2</td></tr> <tr><td>2.1</td></tr> <tr><td>2.2</td></tr> <tr><td>2.3</td></tr> <tr><td>2.4</td></tr> <tr><td>2.5</td></tr> <tr><td>2.6</td></tr> <tr><td>2.7</td></tr> <tr><td>2.8</td></tr> <tr><td>2.9</td></tr> <tr><td>3</td></tr> <tr><td>3.1</td></tr> <tr><td>3.2</td></tr> <tr><td>3.3</td></tr> <tr><td>3.4</td></tr> <tr><td>3.5</td></tr> </table>				2	2.1	2.2	2.3	2.4	2.5	2.6	2.7	2.8	2.9	3	3.1	3.2	3.3	3.4	3.5
	2																								
	2.1																								
	2.2																								
	2.3																								
	2.4																								
	2.5																								
	2.6																								
	2.7																								
	2.8																								
	2.9																								
	3																								
	3.1																								
	3.2																								
	3.3																								
	3.4																								
	3.5																								
	25.7		118.6		4.2																				
	18.11		85.5		2.6																				
	12.85		60.46		1.32																				
9.40	43.8	0.52																							
7.19	33.35	0.16																							
5.77	26.6	0.14																							
4.85	22.24	0.16																							
4.21	19.35	0.16																							
3.77	17.25	0.13																							
3.25	15.64	0.14																							
3.01	14.46	0.13																							
2.83	13.53	0.12																							
2.68	12.78	0.112																							
2.56	12.16	0.091																							
2.46	11.63	0.082																							
2.37	11.18	0.084																							
2.29	10.79	0.081																							
2.23	10.45	0.09																							
2.17	10.14	0.12																							

THD is an amplitude parameter, so 0.1% THD == 60 dB SINAD

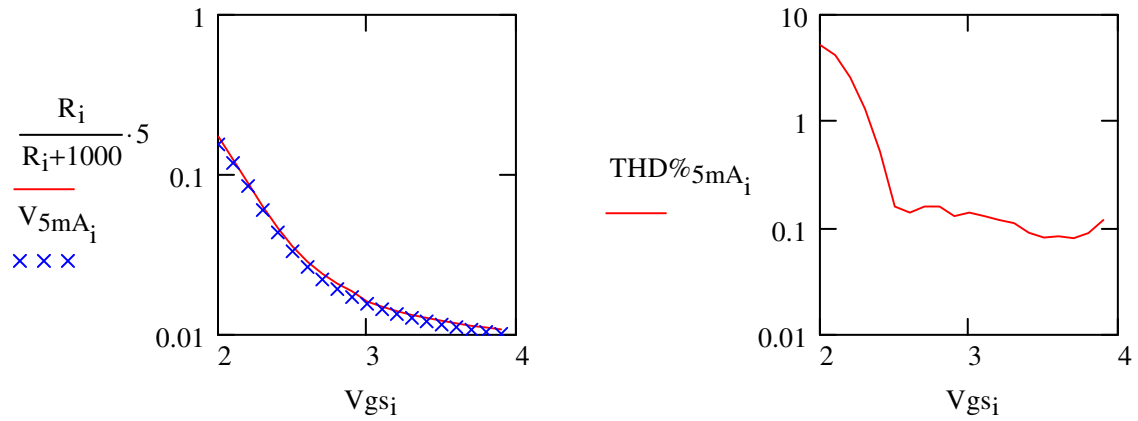5 mA peak current--this is more than we'd ever actually have






The distortion is significant up to $V_{gs}=2.4$ V, but that's a 9-ohm resistance.

Now let's look at the 1 mA peak current numbers

$j := 1..10$

$V_{gs2} :=$	$R :=$	$V_{1mA} :=$	$\cdot mV$	$THD\%_{1mA} :=$
$\begin{pmatrix} 2.0 \\ 2.2 \\ 2.4 \\ 2.6 \\ 2.8 \\ 3 \\ 3.3 \\ 3.6 \\ 3.9 \end{pmatrix}$	$\begin{pmatrix} 36.17 \\ 18.11 \\ 9.40 \\ 5.77 \\ 4.21 \\ 3.25 \\ 2.68 \\ 2.37 \\ 2.17 \end{pmatrix}$	$\begin{pmatrix} 7.73 \\ 6.53 \\ 4.32 \\ 3.10 \\ 2.44 \\ 2.07 \\ 1.754 \\ 1.567 \\ 1.441 \end{pmatrix}$		$\begin{pmatrix} 0.073 \\ 0.1022 \\ 0.036 \\ 0.023 \\ 0.026 \\ 0.028 \\ 0.018 \\ 0.012 \\ 0.014 \end{pmatrix}$

$ii := 0..rows(V_{gs2}) - 1$

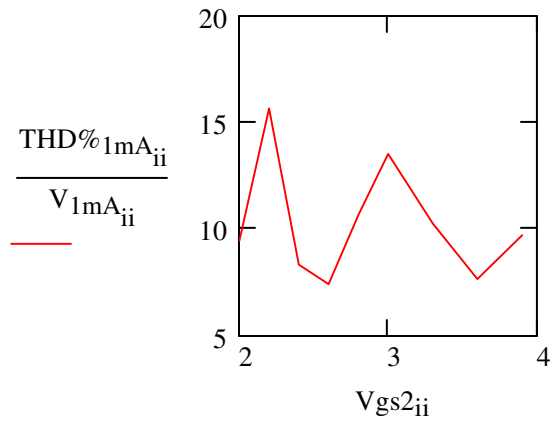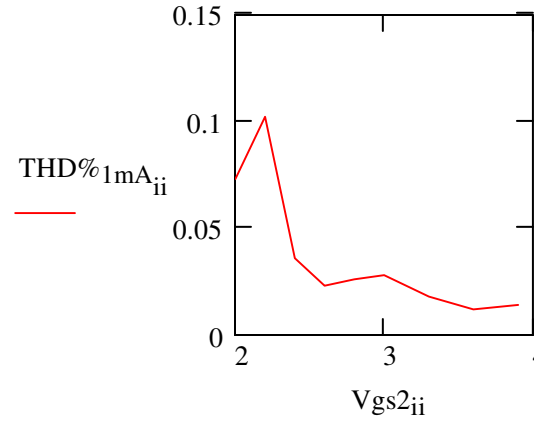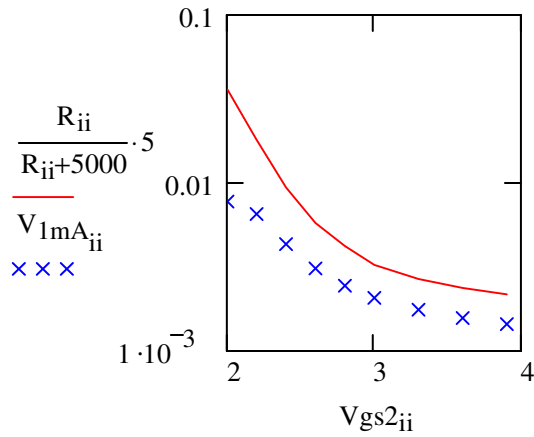

The wisdom here is that 2N7000s don't behave like JFETS--you have to bypass the gate to the drain, not to $(V_g+V_d)/2$. The difference is pretty big--more than 15 dB in the distortion. For a practical device, probably a 20:1 voltage divider is OK (e.g. 2M:100k--that won't cause a lot of offset error with 5 ohms).

