

Robert Hickey  
11/12/97

**Extracting Scattering Parameters from SPICE**


Scattering, or S parameters are easily generated by an AC analysis in SPICE. S parameters are defined with respect to incident (a1 and a2) and reflected (b1 and b2) voltage waves defined by the diagram below and by:

$$a1 = (V1 + Z0 * I1) / (2 * \text{SQRT}(Z0)) \quad (\text{Eq. 1})$$

$$b1 = (V1 - Z0 * I1) / (2 * \text{SQRT}(Z0)) \quad (\text{Eq. 2})$$

$$a2 = (V2 + Z0 * I2) / (2 * \text{SQRT}(Z0)) \quad (\text{Eq. 3})$$
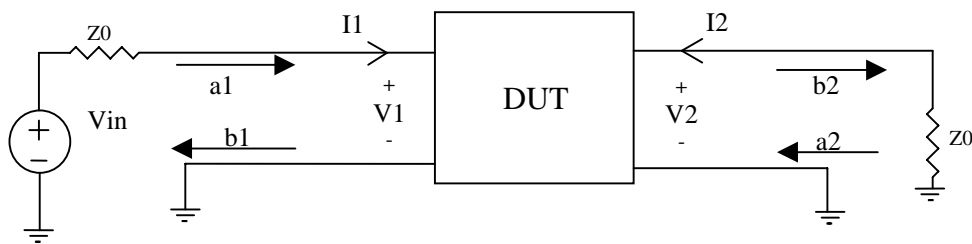
$$b2 = (V2 - Z0 * I2) / (2 * \text{SQRT}(Z0)) \quad (\text{Eq. 4})$$



The scattering matrix relates the incident and reflected waves.

$$(\text{Eq. 5}) \quad \begin{bmatrix} b1 \\ b2 \end{bmatrix} = \begin{bmatrix} S11 & S12 \\ S21 & S22 \end{bmatrix} \begin{bmatrix} a1 \\ a2 \end{bmatrix}$$

$S11 = b1/a1$  for the case when  $a2 = 0$ .  $a2$  is the wave reflected from the load back toward the output port and is zero when the load is the impedance used to define the S parameters. Hence,

$$(\text{Eq. 6}) \quad S11 = \frac{V1 - Z0 * I1}{V1 + Z0 * I1}$$

Noting that  $Z1 = Zin = V1/I1$ , we have the familiar

$$(\text{Eq. 7}) \quad S11 = \frac{Z1 - Z0}{Z1 + Z0}$$

Let the Voltage Source be 2 Volts. This value simplifies calculations without compromise, for an AC run in SPICE is a small signal analysis. The voltage at the network input is then found from a voltage divider as:

$$V1 = (2 * Z1) / (Z1 + Z0) \quad (\text{Eq. 8})$$


Solving for  $Z1$  in terms of  $V1$  results in:

$$Z1 = (V1 * Z0) / (2 - V1) \quad (\text{Eq. 9})$$

Substituting this in Eq. 7 yields the simple result:

$$S11 = V1 - 1 \quad (\text{Eq. 10})$$

This is more intuitive than many S parameter results. If a 2 volt source is used at the input, and if the input is perfectly matched, V1 will be 1 Volt. Subtracting 1 from that leaves S11 of zero, a “proper” result for a perfect impedance match. In SPICE, 1 is easily subtracted from V1 by attachment of a 1 Volt AC generator to the V1 node. The voltage at node 11 below is S11 in both magnitude and phase.

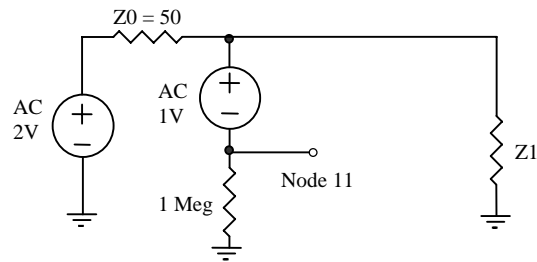

S21, the forward scattering parameter, is defined as  $S_{21}=b_2/a_1$ . Using equations 1 and 4, this becomes

$$S_{21} = (V_2 - I_2 * Z_0) / (V_1 + I_1 * Z_0) \quad (\text{Eq. 11})$$

S21 is defined by Eq. 11 for the case when there is no reflection from the load, setting  $a_2 = 0$ . This produces  $I_2 = -V_2/Z_0$ , and Eq. 11 reduces to

$$S_{21} = (2 * V_2) / (V_1 + Z_0 + I_1) \quad (\text{Eq. 12})$$


Consider our special case for a 2 volt driving generator.  $I_1$ , the input current, is related to the input voltage,  $I_1 = V_1 / Z_1$ . Substitution into Eq. 12 yields

$$S_{21} = (2 * V_2 / V_1) / (1 + Z_0 / Z_1) \quad (\text{Eq. 13})$$

Equation 9 relates  $Z_1$  to  $V_1$ ; substitution simplifies to the almost trivial result that

$$S_{21} = V_2 \quad (\text{Eq. 14})$$

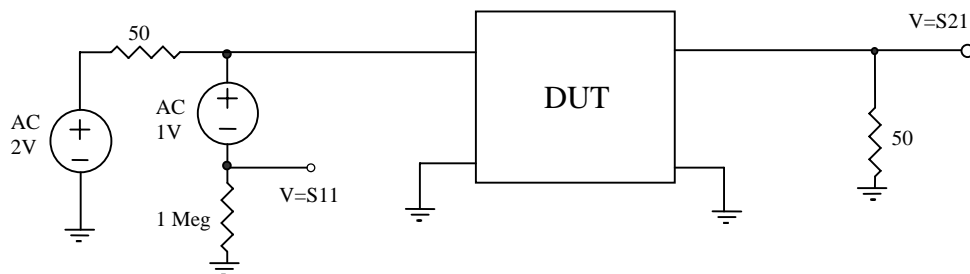Hence, S21 and S11 are calculated in SPICE from



S12 and S22 are calculated with similar ease with

