

# **Electro-Optical Kluges and Hacks**

**A Lab Rat's Guide to Good Measurements**

Phil Hobbs,  
IBM T. J. Watson Research Center  
Yorktown Heights NY



# Hacks Of The Day



- Quantum detection
- A little noise theory
- Low noise front ends
  - ▶ Design tricks and circuit hacks
  - ▶ Detailed example: bootstrapped cascode TIA
- Noise Cancellers & Their Relatives
  - ▶ Motivation
  - ▶ Details
  - ▶ Other linear combinations (locking a laser to an etalon)
- High-Performance Pyroelectrics
  - ▶ Low speed wins!
- Higher speed
  - ▶ Impedance transformation: transformers, reactive networks, constant-resistance T-coils

# Quantum Detection (Optical View)

- One photon gets you one electron ( $\eta \sim 1$ )
- Shot noise is the intrinsic limit (*pace* squeezers)
- $N$  photons/s gives 0 dB SNR in  $N/2$  Hz, max
- Signal and spurious junk are inseparable after detection
- **Etendue ( $n^2 A \Omega$ ) management** for speed and low noise:
  - ▶ Achievable BW goes as average radiance ( $\text{W}/\text{cm}^2/\text{sr}$ )
  - ▶ Leakage, background, and capacitance go as the area
  - ▶ Reduce area, increase NA, consider immersion lens
  - ▶ High current density ( $>10 \text{ mA}/\text{cm}^2$ ) causes nonlinearity
  - ▶ (And, just between you and me: small detectors are *really* hard to align)
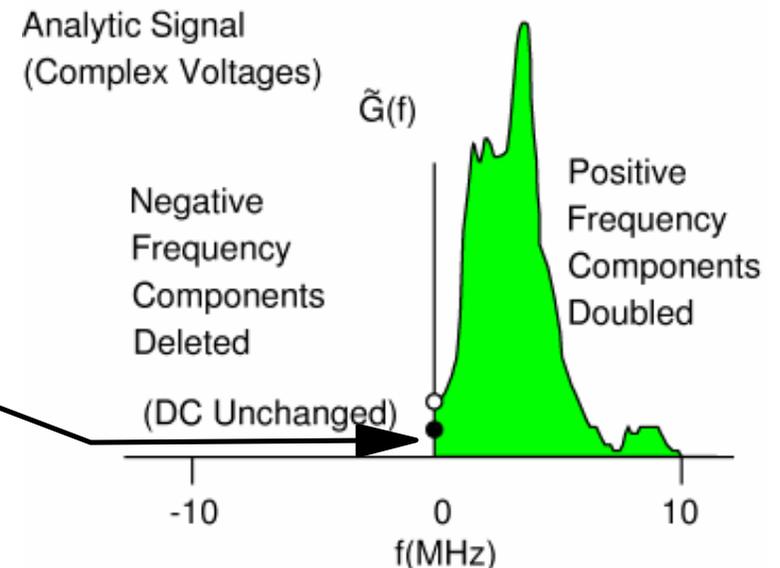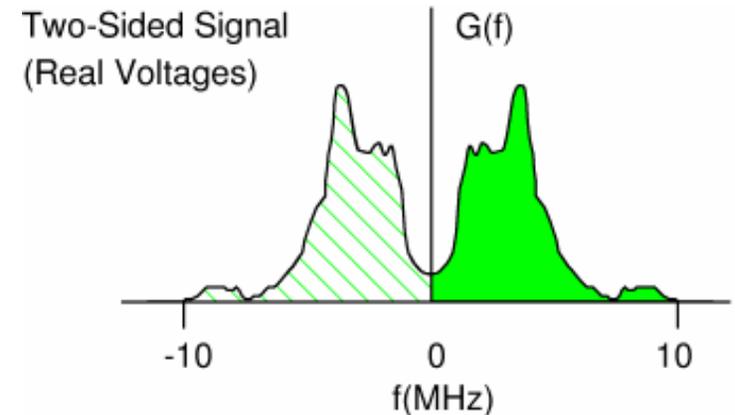
# Analytic Signals

- Circuits people use one-sided BW
- Analytic signal convention
  - ▶ Measurable quantities are real-valued
  - ▶ Analysis is easier in complex exponentials
- Analytic signal definition
  - ▶ Double signal at  $f > 0$
  - ▶ Leave DC alone
  - ▶ Chop off all  $f < 0$
  - ▶ A bit problematic at DC
- Causes mysterious factors of 2:
  - Mean square AC power doubled
  - 1-s boxcar has 0.5 Hz noise BW
  - $N^{1/2}$  in 1s is  $(2N)^{1/2}$  in 1 Hz!



# Noise Physics

## ■ Johnson Noise:

- ▶ Classical equipartition & fluctuation-dissipation theorem
- ▶ Johnson noise PSD  $p_{NJ} = kT$  J/s/Hz when matched
  - $v_N = (4kTR)^{1/2}$ ,  $i_N = (4kT/R)^{1/2}$  in 1 Hz (unmatched)
  - Noise temperature  $T_N = T_{amb}$  (resistor),  $T_N \ll T_{amb}$  (LNA)

## ■ Shot Noise:

- ▶ Photodetection is a Poisson process: variance = mean
- ▶ Shot noise limit:  $i_{Nshot} = (2eI_{dc})^{1/2} > (4kT_N/R)^{1/2}$  when:
  - Signal drops 50 mV across  $R_L$  (300K)
  - Signal power  $> 7 \mu\text{W}$  in  $50\Omega$  (very quiet amp [35K])
- ▶ **NB: It's easy to make currents with no shot noise (metal resistor)**
- ▶ Pauli principle forces electrons to be highly correlated: noise power suppression is  $\sim (\text{mean free path})/(\text{length of resistor})$

## ■ Technical noise (stay tuned)

# Noise Definitions

- Noise statistics are ensemble averages or short-time averages
  - ▶ They can be time-varying
- Signals at different frequencies add in power since beat term averages to zero
- Noise best specified as power spectral density (PSD): for reasonable bandwidths, think of this as noise in 1 Hz BW
  - ▶  $p_N$  is PSD,  $P_N$  is total noise power
- Noise Bandwidth:
  - ▶  $BW_N = (\text{total noise power}) / (\text{peak noise PSD})$
  - ▶ Equivalent width of power spectrum
  - ▶  $BW_N = 1 / (\text{autocorrelation width of impulse response})$
  - ▶ Generally wider than 3 dB BW ( $\pi/2$  times for RC rolloff)

# Quantum Detection (Circuit View)

- **Output Current:**
  - ▶ consists of **N Poissonian pulses/s** regardless of QE and  $I_{\text{dark}}$
  - ▶ **Gain can't fix this (PMTs just give bigger pulses)**
- All fundamental noise sources are white
- **Circuit Model:** current source shunted by  $C_d$ 
  - ▶  $C_d \sim 100 \text{ pF/cm}^2$  for a good PIN device, fully depleted
- **Square law device:**
  - ▶  $P_{\text{opt}} = hnN$ ,  $P_{\text{el}} = (eN)^2 R_L$
  - ▶ **Electrical power theoretically unlimited as  $R_L \Rightarrow$  infinity**
  - ▶ Johnson noise is always  $kT/s/Hz$ : weak signals are easily swamped

# Detection Regimes (Quiet Source)

- **Photon counting:**
  - ▶  $N < 10^8$  photons/s (40 pW @ 500 nm)
  - ▶ Use PMT or Geiger-mode APD (< 1 MHz)
  - ▶ Useful BW (20 dB SNR)  $\sim N / 200$
- **Shot-noise limited:**
  - ▶  $I_d R_L > 50$  mV @300K
  - ▶ Can always get there with bigger  $R_L$  (Si, InGaAs) but BW suffers
- **Otherwise Johnson-limited:**
  - ▶ Nice quiet photoelectrons are immersed in circuit noise
  - ▶ Circuit constants are the problem
  - ▶ **Circuit hacks can be the solution**

# Escaping Johnson Noise

- Additive circuit noise swamps photoelectrons
  - ▶ Very wasteful--we've paid a lot for those photons!
- 3 dB SNR improvement can save:
  - ▶ Half the laser power needed
  - ▶ Half the measurement time required
  - ▶ Half the cost and 2/3 the weight of the optical system
- To escape Johnson
  - ▶ Smaller detectors, higher bias (reduces  $C$ )
  - ▶ Low noise amplifiers (reduces noise)
  - ▶ Electron multiplying detectors or cooled CCDs (increases signal)
  - ▶ Impedance transformation networks (increases signal)
  - ▶ Other circuit hacks

# Example:

## Low-Level PIN Photodiode Front End

### ■ Design Parameters:

- ▶ Bandwidth:  $B \geq 1$  MHz
- ▶ Obese  $1 \text{ cm}^2$  Si PIN Photodiode,  $C_d = 100$  pF (fully depleted)
- ▶ Photocurrent:  $i_{\text{phot}} = 2 \mu\text{A}$ 
  - Photon arrival rate  $N = i_{\text{phot}}/e = 12.4$  THz
- ▶ SNR: Within 2 dB of shot noise limit
  - Maximum SNR =  $N/2B = 68$  dB in 1 MHz

# Front End Choices

- Load resistor
- Transimpedance amplifier
- Bootstrap + load resistor
- Cascode transimpedance amp
- **Bootstrapped cascode TIA**

# Load Resistor

- **First Try**

- ▶  $R_L = 1 \text{ M}\Omega$  : BW = 1600 Hz (ick)

- **Everything is wired in parallel:**

- ▶ Signal and noise roll off together
  - ▶ SNR constant even though signal rolls off by 55 dB

- ▶ Subsequent amplifier limits SNR



- **Optimization:**

- ▶ Lower  $R$  increases BW, but SNR drops due to Johnson noise

- ▶ Shot = Johnson when  $IR = 2kT/e$  (~50 mV@300K)



- ▶ **Optimum  $R$  drops ~ 200 mV**

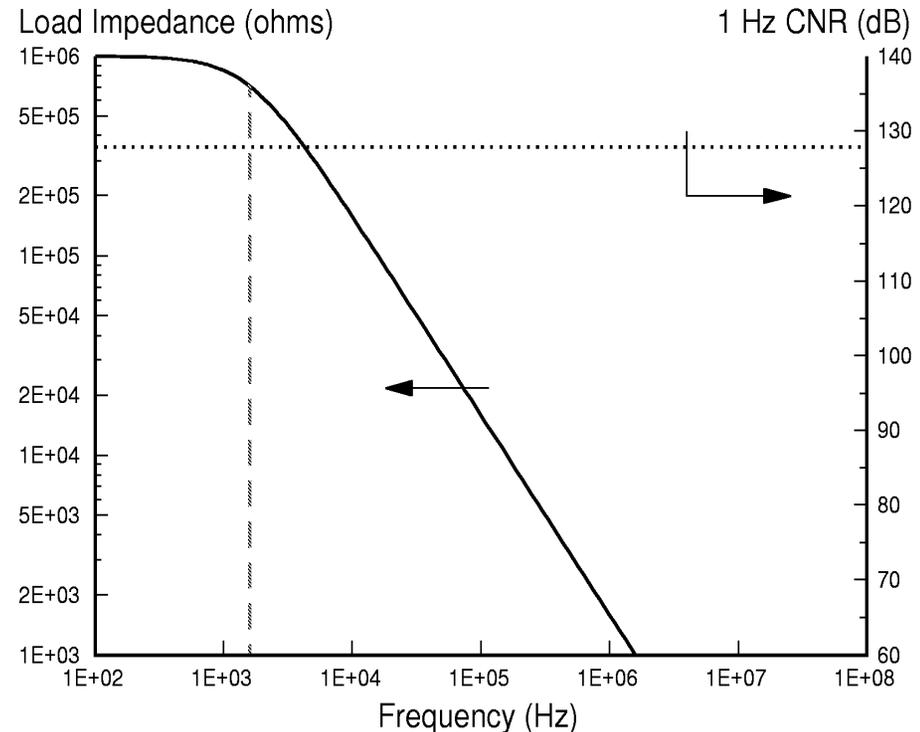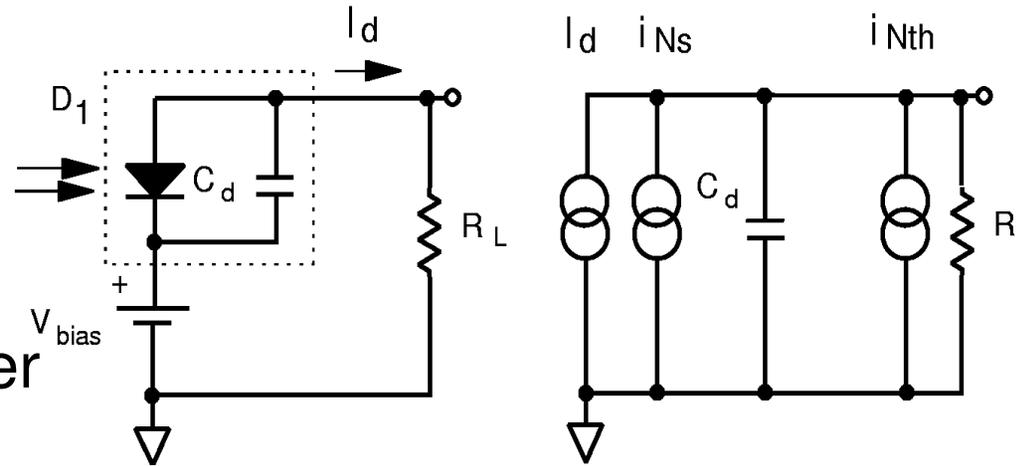- ▶  **$R_{\text{opt}} = 100\text{k}$ , BW = 16 kHz**


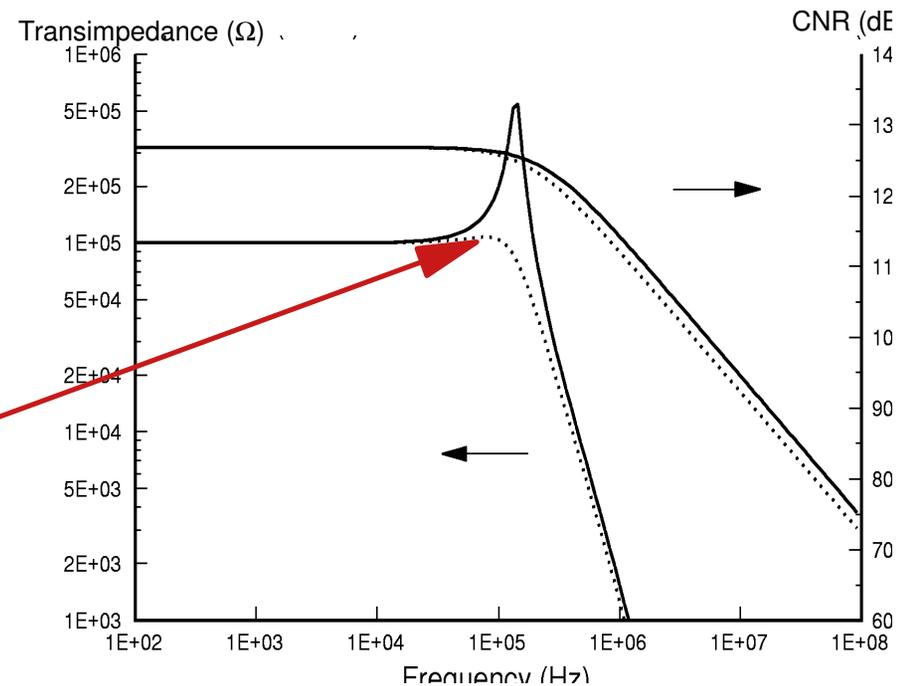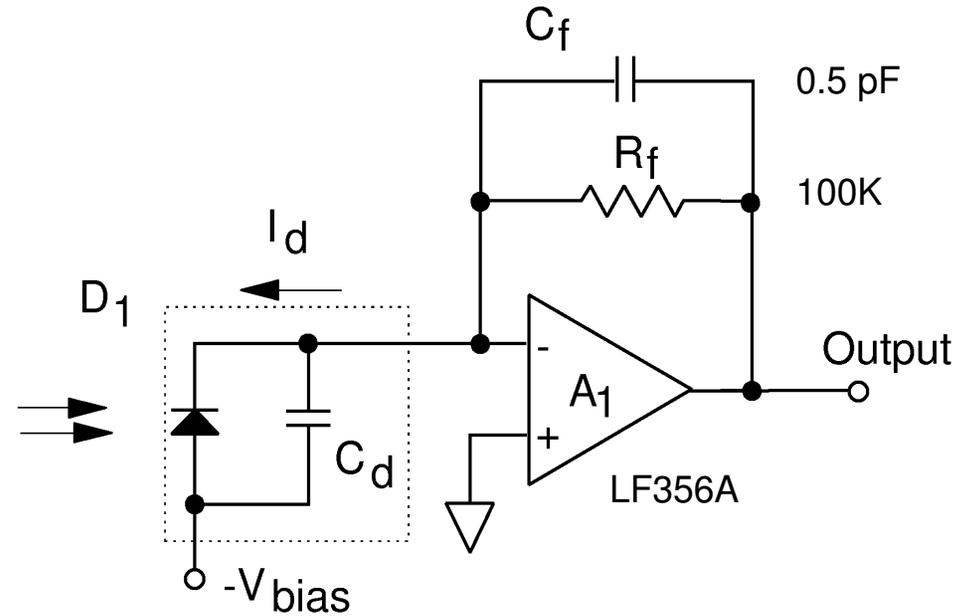
# Transimpedance Amp

- Connect PD to virtual ground
  - ▶ Op amp wiggles output end of  $R_F$  to keep input end still
- Improves BW but not SNR
  - ▶ 3 dB BW  $\sim 0.5(f_{RC} * GBW)^{1/2}$
- Unity gain stability unnecessary
- Big improvement but don't push it too much:
  - ▶ Noise and instability problem due to capacitive load on summing junction
  - ▶ Fast amplifiers are worst
- 0.5 pF  $C_f$  helps instability but can't fix SNR problem




# Transimpedance Amp

## ■ Transimpedance BW

- ▶ Less than closed-loop BW
- ▶ Depends on values not ratios
- ▶ Actual BW obtained depends on frequency compensation


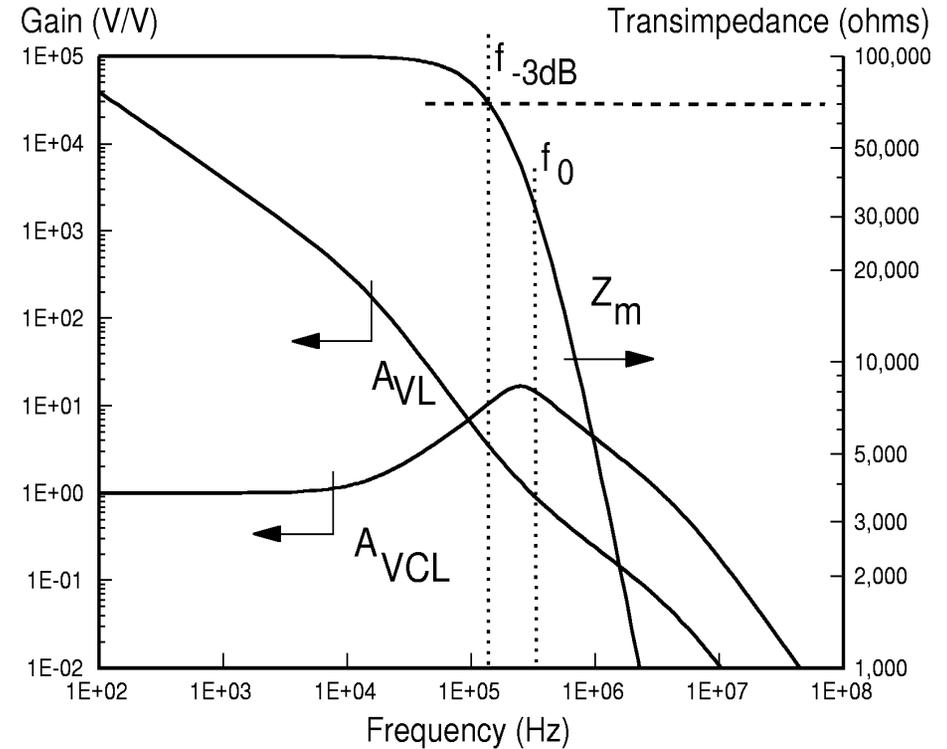
## ■ Low noise

- ▶ Amplifier noise dominates at large  $R_f$
- ▶ Active devices can have  $T_N \ll 300K$  ( $T_N = e_{NiN} / 4k$ )
- ▶ ~ 10K for good bipolar op amps
- ▶ Even lower for FETs but needs inaccessible impedance levels



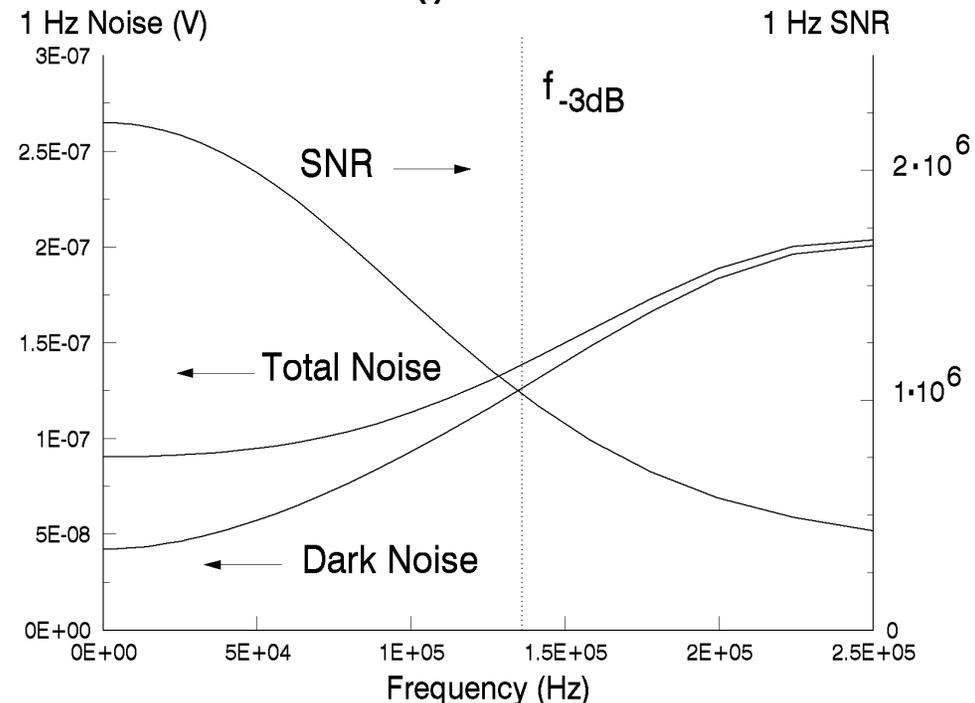
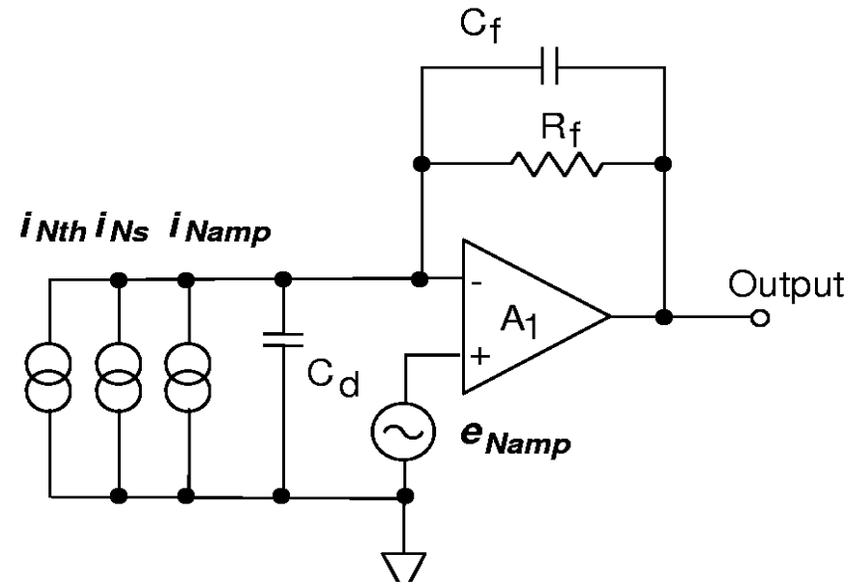
# DIY Op Amps

- Current noise of op amp appears in parallel with  $I_{\text{phot}}$ 
  - ▶ Treated just like signal: no high freq SNR penalty
- Voltage noise of op amp sees *full noninverting gain*
  - ▶ Big noise spike at high freq, due to  $C_d$  (differentiator)
- Reducing  $e_{Namp}$  means running the input stage at higher bias
  - ▶ add a BJT stage to the front
  - ▶ Increases  $i_{Namp}$ , but that's OK


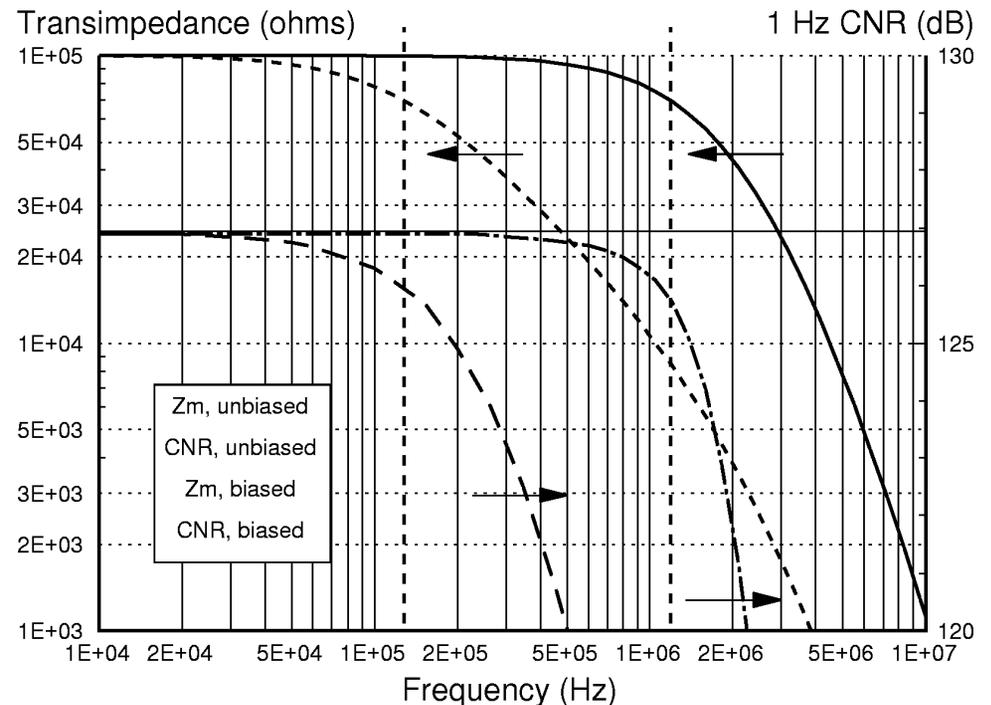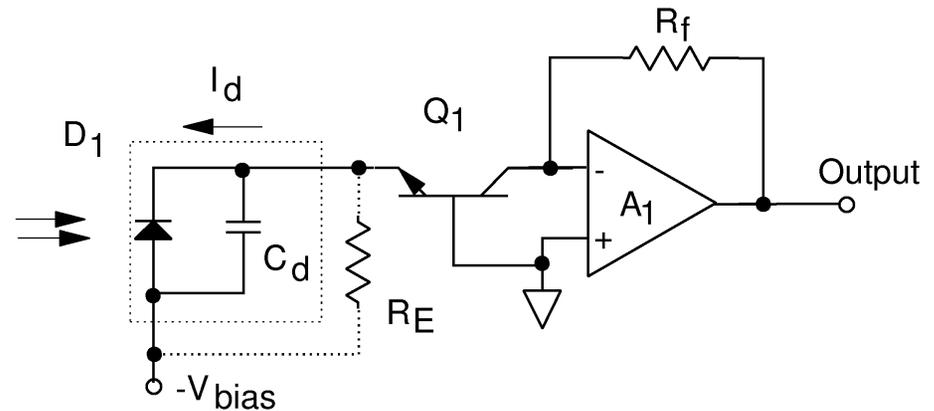
# Cascode TIA

- Isolate  $C_d$  from summing junction with cascode  $Q_1$ 
  - ▶ BW limited by emitter impedance  $r_E = 1/g_m$
  - ▶  $BW(\text{Hz}) = 6.2 I_C / C_d$
- Biasing cascode with sub-Poissonian  $I_{\text{bias}}$  reduces  $r_E$  --improves BW
  - ▶ Noise now limited by  $R_{b'}$  and shot noise of  $I_b$
  - ▶ Noise multiplication much reduced compared to TIA



# Bootstrapping

- Bootstrap transistor

- ▶ Follower forces cold end of  $D_1$  to follow hot end
- ▶ No voltage swing  
->no capacitive current

- Speed set by  $r_E C_d$  not  $R_L C_d$

- ▶ 50x faster than RC at  $I_{dc}=300 \mu A$ ,  
 $R_L=100 k\Omega$

- Superbeta transistor


- ▶  $\beta \sim 1000$ : Very low base current noise

- Noise Voltage

- ▶ Limited by  $R_b$  and  $r_E(2eI_C)^{1/2}$



- ▶ Noise multiplication similar to TIA

- Can be applied with other techniques

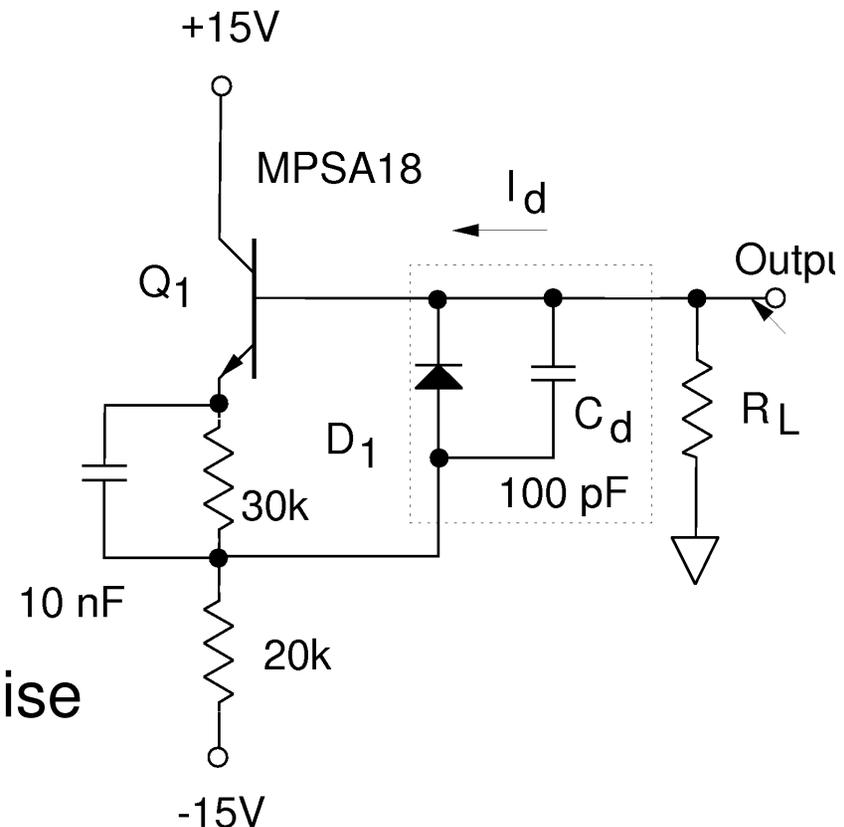

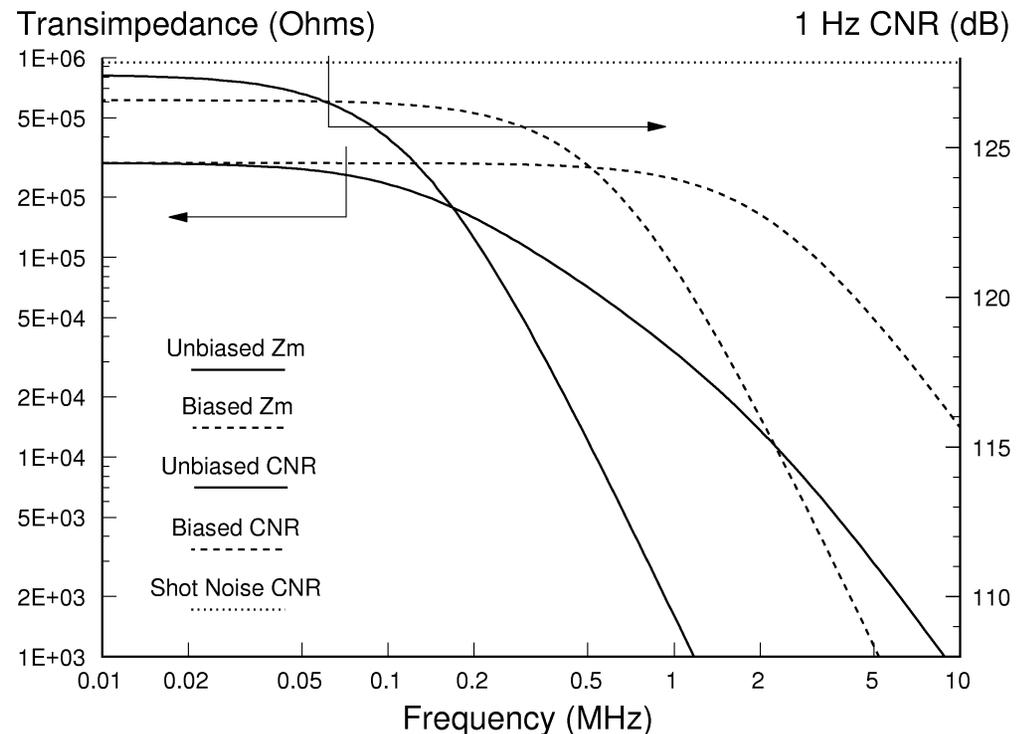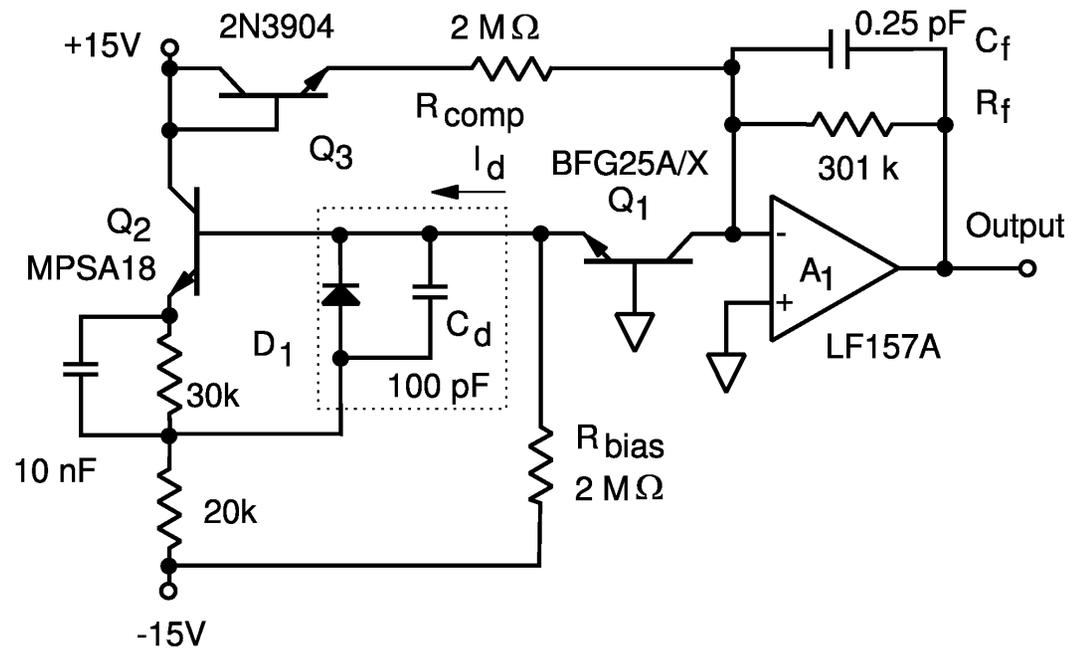
# Bootstrapped Cascode TIA

- Can't use enough  $Q_1$  bias to get 1 MHz BW without being limited by  $I_b$  shot noise and  $R_b$  Johnson noise
- Bootstrap runs at higher current: lower voltage noise
- Reduces effective  $C_d$ 
  - ▶ Superbeta transistor  $Q_2$  has much lower base current shot noise, so can run at higher current than  $Q_1$  without ruining the SNR
  - ▶ Bootstrap can be applied along with cascode


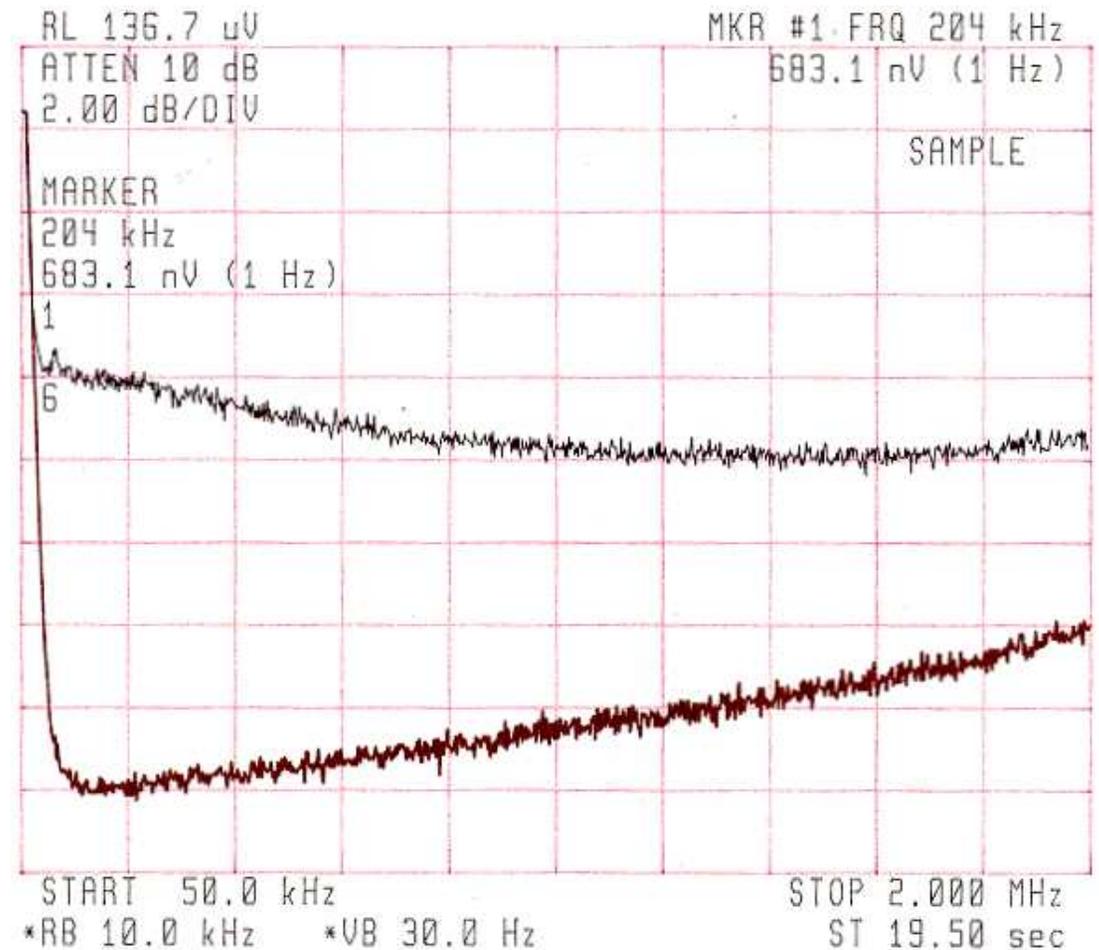
# Bootstrapped Cascode TIA

- **Final performance:**
  - ▶ Within 1 dB of shot noise, DC-1.3 MHz
  - ▶ 600x bandwidth improvement over naive approach
- **Three turns of the crank** to get 1 MHz BW with 100 pF & 2  $\mu$ A
- **Not much more juice available here:**
  - ▶ **optical fix needed next time**



Bottom: Dark noise

Top: 2  $\mu$ A photocurrent

# Detectors With Gain

- **Electron Multiplication:** used in PMTs, APDs, & LLLCCDs
  - ▶ Gain applied to electrons before front end amplifier
  - ▶ Front end noise contribution reduced by  $M$
  - ▶ Allows low load resistances => **increased BW**

**HOWEVER,...**

- ▶ Gain inherently noisy (at least 3 dB noisier than PIN)
  - ▶ Other tradeoffs depend on device (e.g. GBW of APD)
- **Shot noise doesn't improve:**
  - ▶  $N$  photons per second gives 0 dB SNR in  $N/2$  Hz, max
  - ▶ Gain amplifies noise along with signal

# Noise Physics Again


- Technical Noise
  - ▶ Usually dominant in laser measurements, especially bright field
  - ▶ Dominates in large-signal limit ( $\rho_N \sim P_{\text{opt}}^2$ )
  - ▶ Laser RIN, demodulated FM noise, wobble noise, below-threshold side modes, mode partition noise, coherence fluctuations microphonics,  $1/f$  noise, noisy background, phase of the moon, pink elephants,.....
- Many strategies for getting round it, such as:
  - ▶ Reduce background: Dark field and dim field
  - ▶ Move to high frequency: Heterodyne interferometers
  - ▶ Move at least a little away from DC: Chopping
  - ▶ Compare beam before and after sample: Differential detection
  - ▶ NB: Lots of possibilities, because there's no 100% solution

# Shot Noise

## *Rule of One*

- *One* coherently added photon per second gives an ac measurement with *One* sigma confidence in a *One* hertz bandwidth.
  - ▶ True for bright field or dark field:
  - ▶ **Bright field == dark field, except for technical noise**
    - BF: Source instability (RIN)
    - DF: Johnson noise
  - ▶ DC is actually 3 dB better for a given temporal response, except for the usual baseband suspects
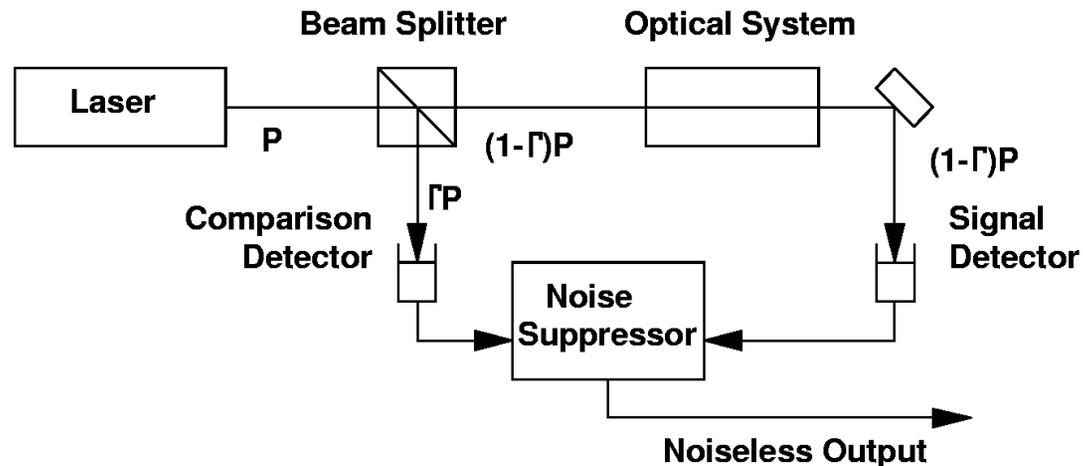
# Differential Detection Ought To Be Perfect




- Apart from shot noise,  $I_{sig}$  and  $I_{comp}$  are perfectly correlated
- Optical systems are extremely linear and wideband
- Photodiodes can also be extremely linear and pretty wideband:

$\Rightarrow I_{sig}/I_{comp} == I_{sig}/I_{comp}$  (differential gain == average gain)

- ▶ If the DC cancels, the noise cancels at all frequencies
- Problem: only works with beams of identical strength:  
Need to ship a grad student with each system to keep it adjusted

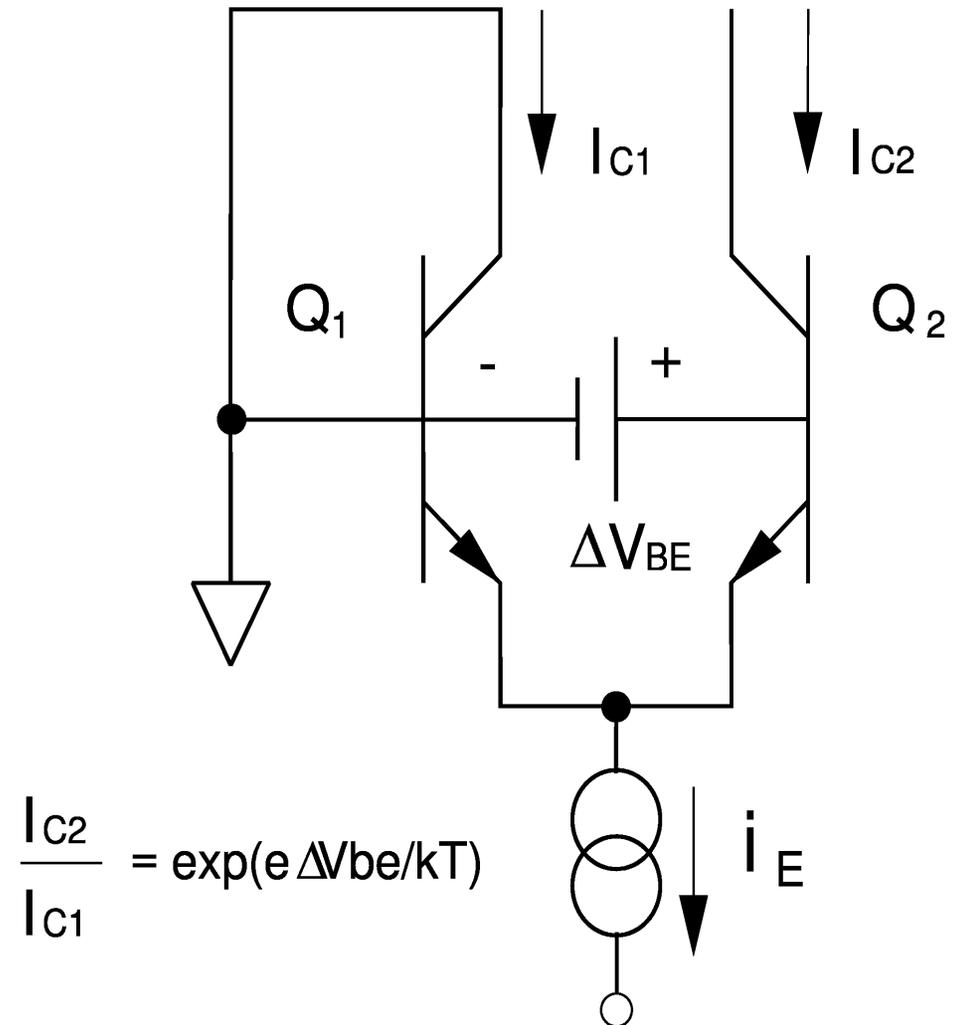
# BJT Differential Pair

- With fixed  $\Delta V_{be}$ , the ratio of  $I_{C2}/I_{C1}$  is constant over several decades of  $I_e$ .
- Linear splitting => fluctuations and DC treated alike
- ( $Q_1$  is in normal bias as shown--the collector can go 200 mV *below* the base before saturation starts)
- Transistors can be fast
- **Adjusting  $\Delta V_{be}$  to null out the photocurrent doesn't disturb the subtraction**


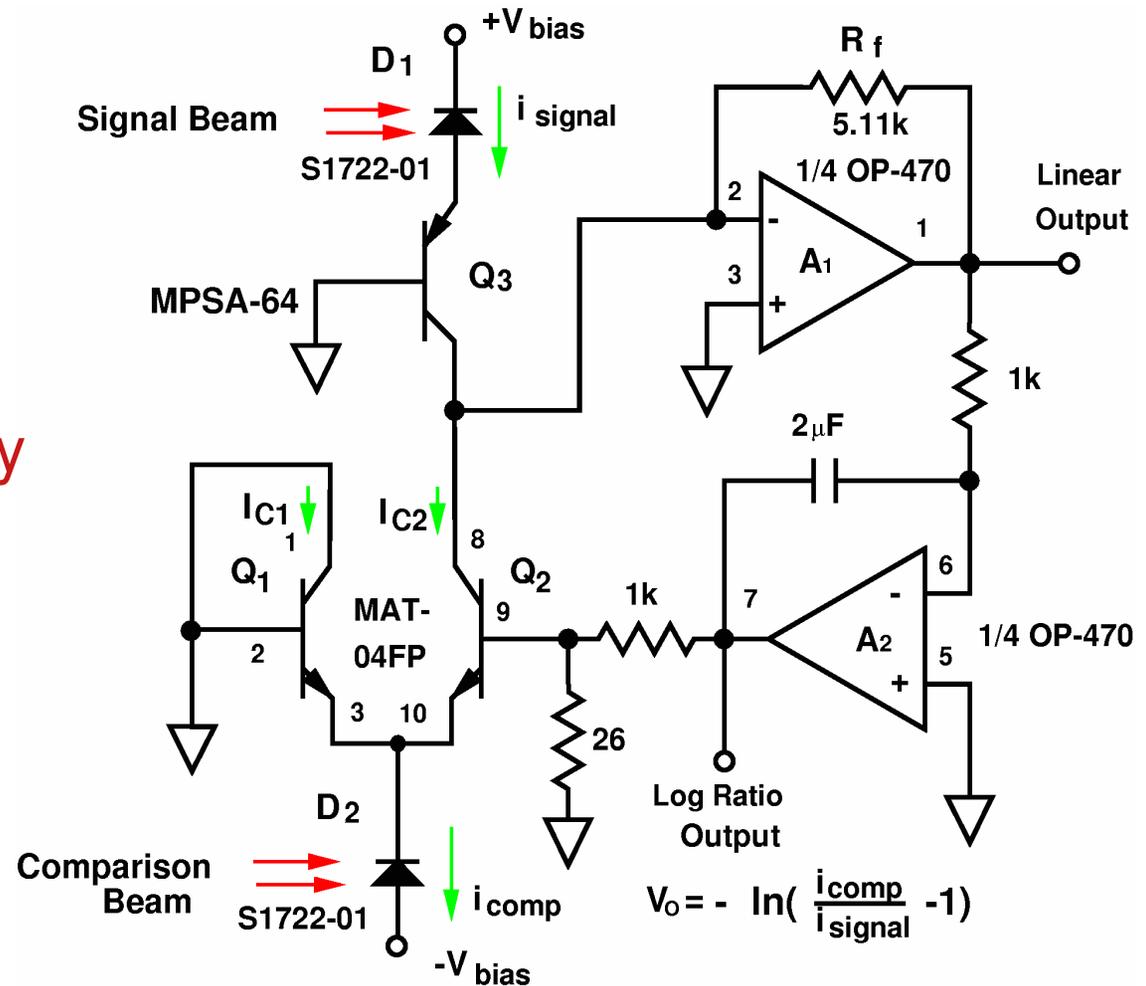
# Basic Noise Canceller

- Add a diff pair to a current-differencing amplifier
- Use feedback control of  $\Delta V_{be}$  to null the DC  
 => **Noise cancels identically at all frequencies**
- Cancellation BW independent of FB BW
- Linear highpass O/P, log ratio LP output ( $\Delta V_{be}$ )
- $1k::26\Omega$  divider gets rid of  $kT/e$  factor in  $\Delta V_{be}$   
 $[2V \iff \exp(1)]$




# Performance: Cancellation

He-Ne showing a strong mode beat (oscilloscope traces)

Upper: TIA mode showing beat waveforms due to 4-wave mixing (comparison beam blocked)

Lower: Cancellation to 0.5 dB above shot noise (comparison beam unblocked)

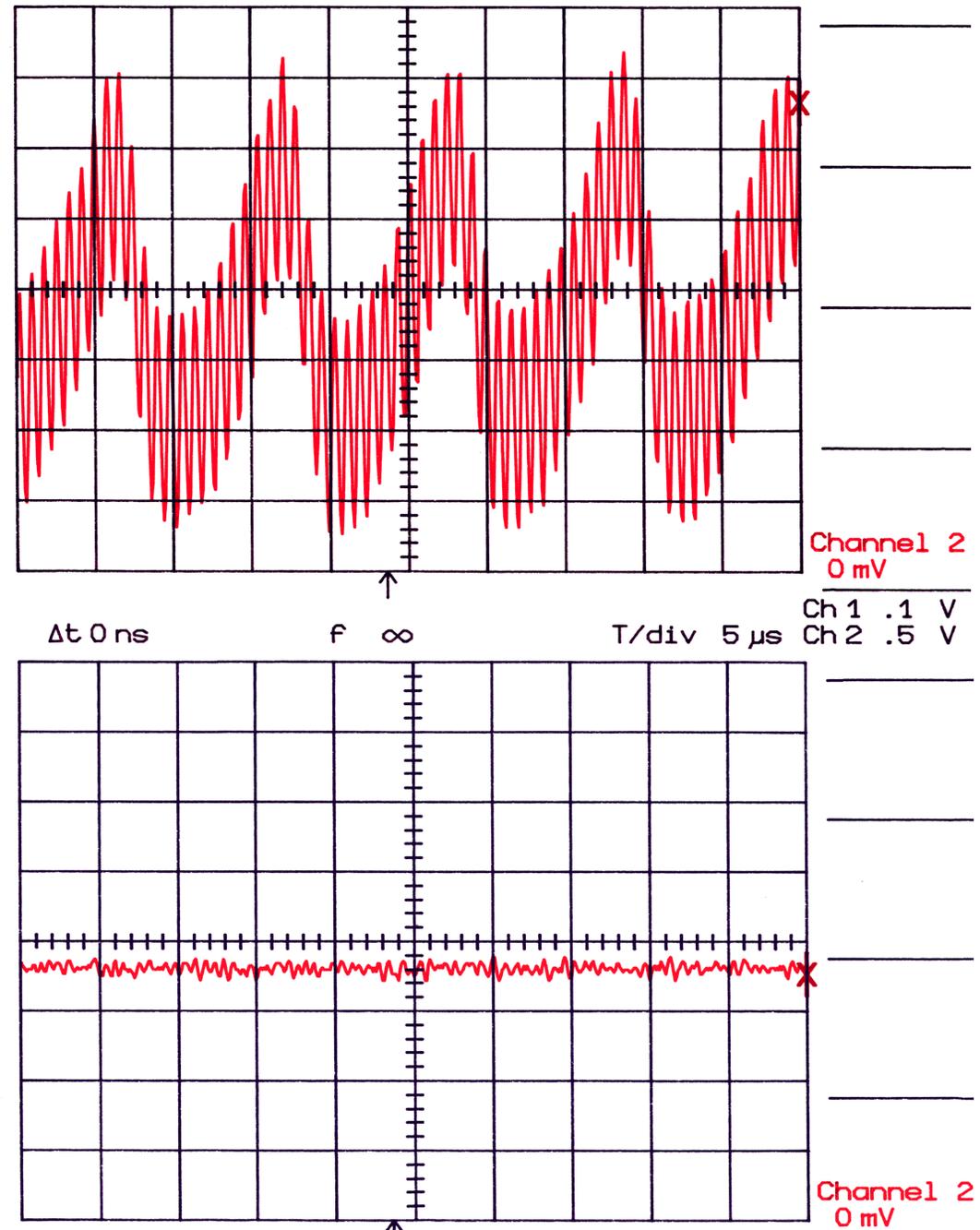
3N3904 discrete BJT  
0.75 mW  $P_{sig}$ , 1.5 mW  $P_{comp}$



# Performance: Cancellation


He-Ne in quiescent period  
 Upper: TIA mode, showing  
 noise and 22 kHz ripple  
 Lower: Cancellation to  
 0.5 dB above shot noise

AVERAGE COMPLETE

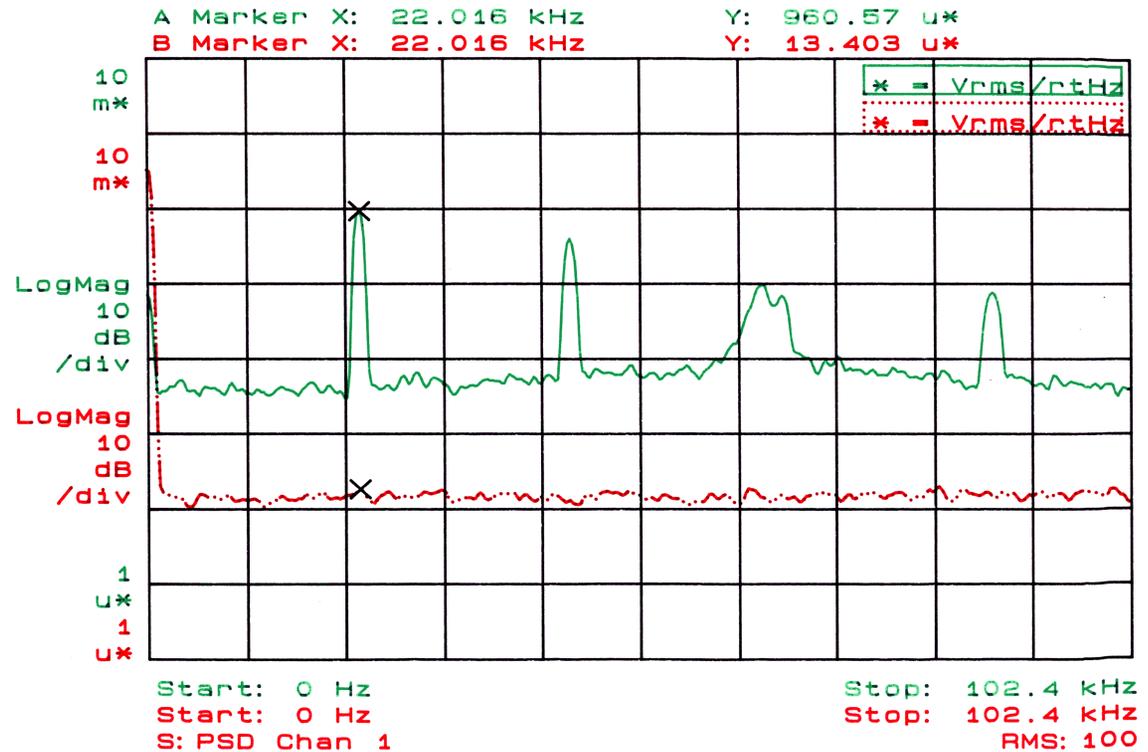




Envelopes of 100 scans,  
 showing mode beats sweeping  
 Upper: TIA mode  
 Lower: >50 dB cancellation,  
 even with multiple modes

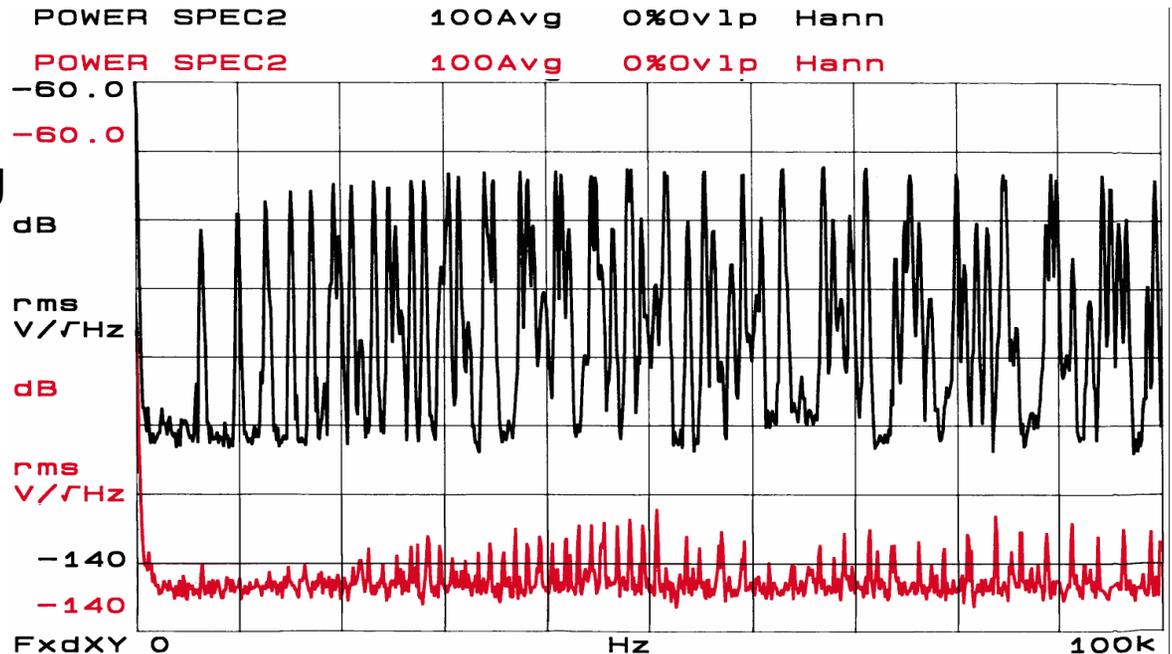3N3904 discrete BJTs  
 0.75 mW  $P_{sig}$ , 1.5 mW  $P_{comp}$




# Performance: Cancellation

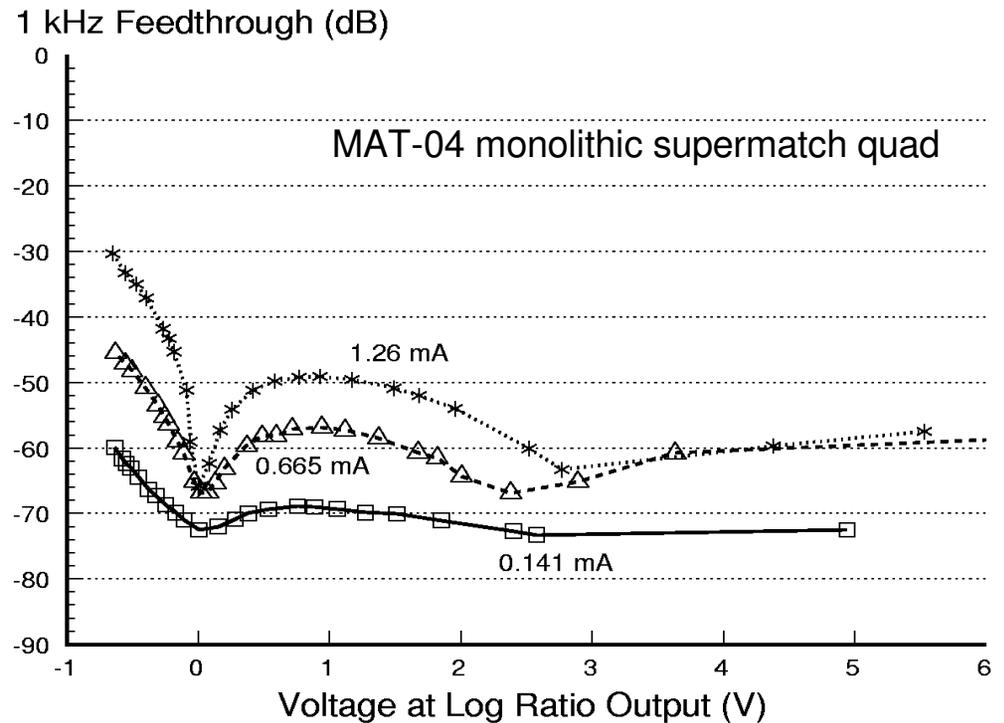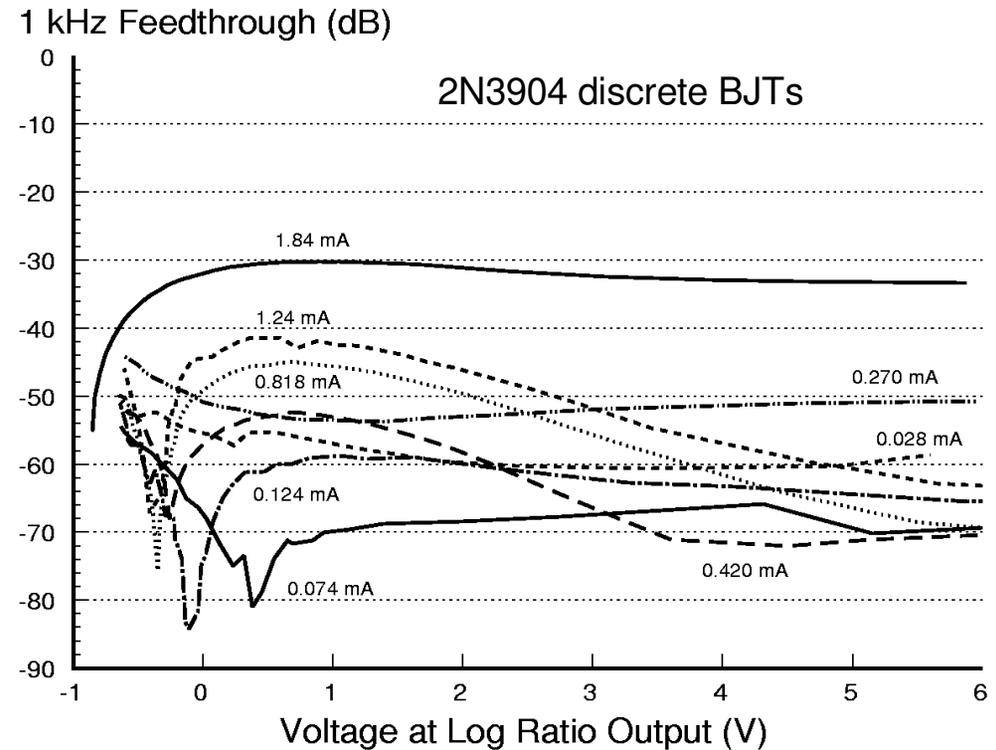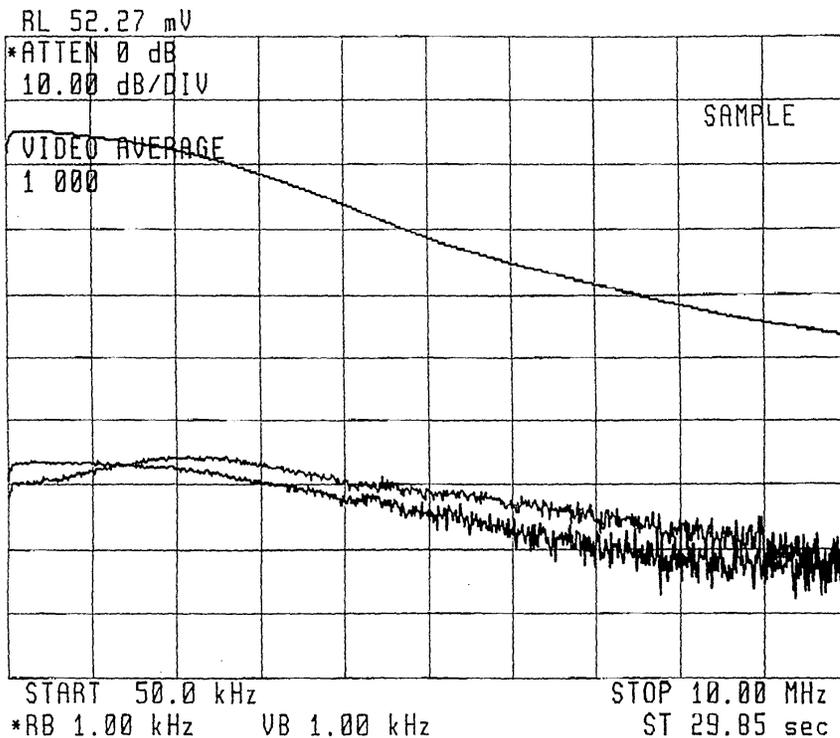- 50-70 dB RIN reduction at low frequency, ~40 dB to 10 MHz
- No critical adjustments
- Cancellation at high currents limited by differential heating



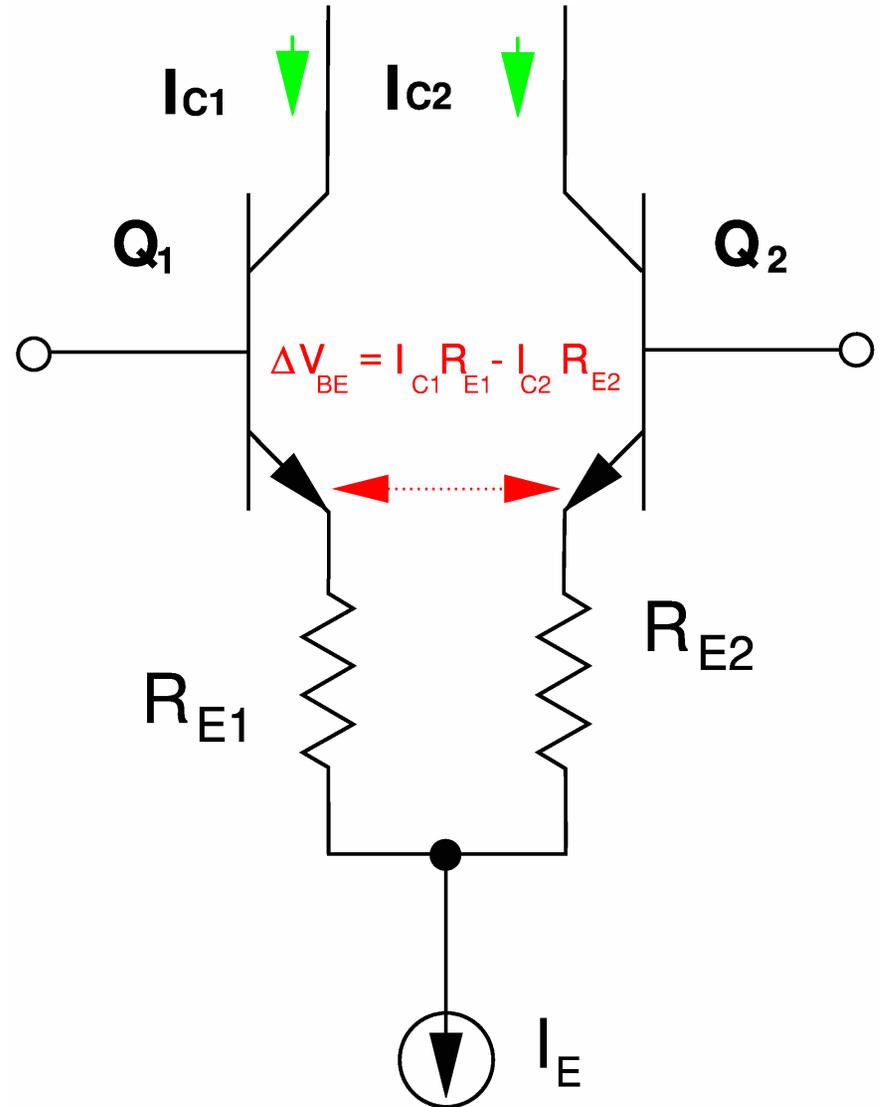
# $R_E$ Degeneration

- Discretes run at different  $T$   
=> Less cancellation at high  $I_C$ 
  - ▶ Use monolithic matching
- Main remaining limit is failure of BJT's to be exponential at high currents
  - ▶  $R_E$  produces negative feedback on emitters, tending to even out the current split
  - ▶ Apply positive FB to the bases, keeping intrinsic  $V_{BE}$  constant




# RE Compensator

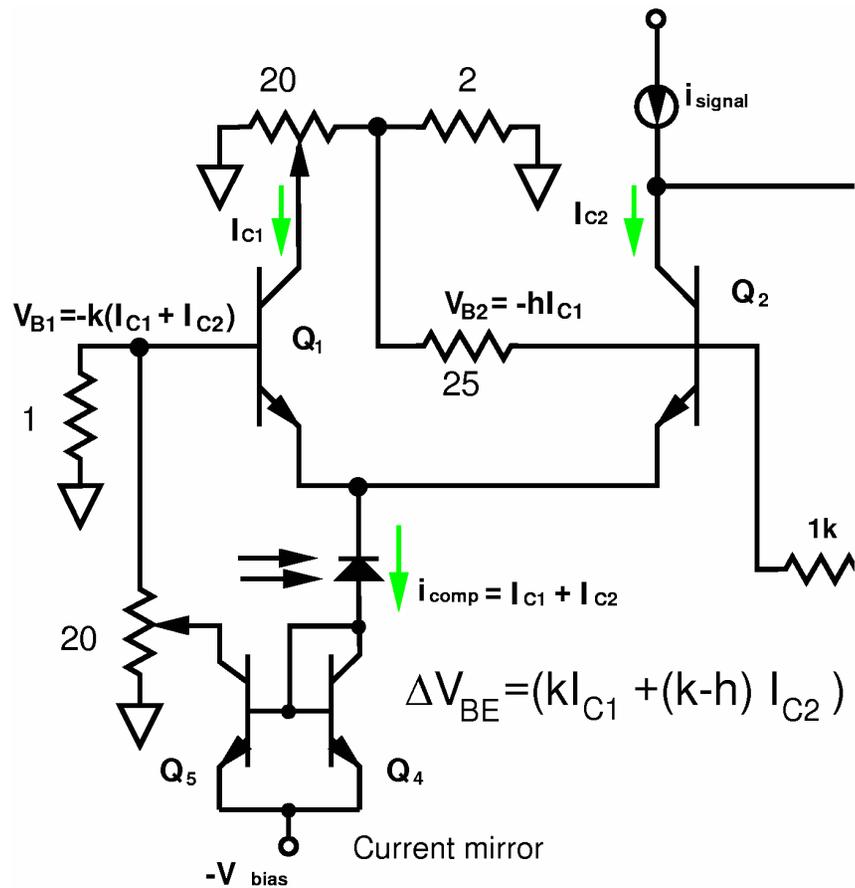


- Requires a current mirror plus a few extra resistors
- Flattens out rejection curve, 10-25 dB improvement

1 kHz Feedthrough (dB)


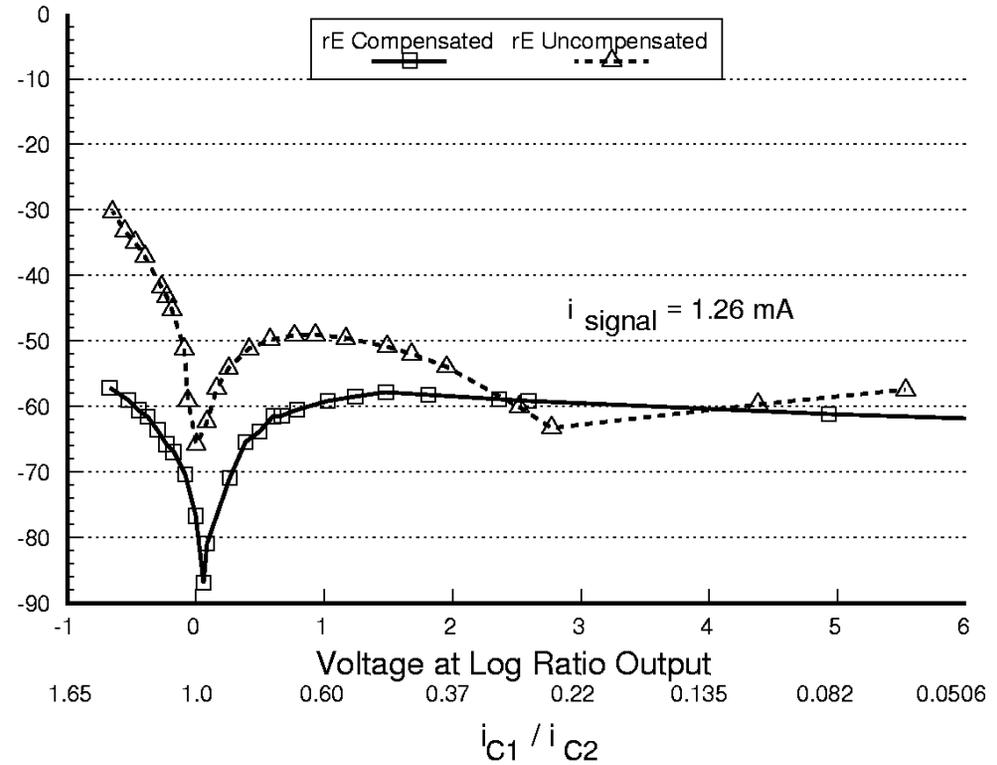


1 kHz Feedthrough (dB)

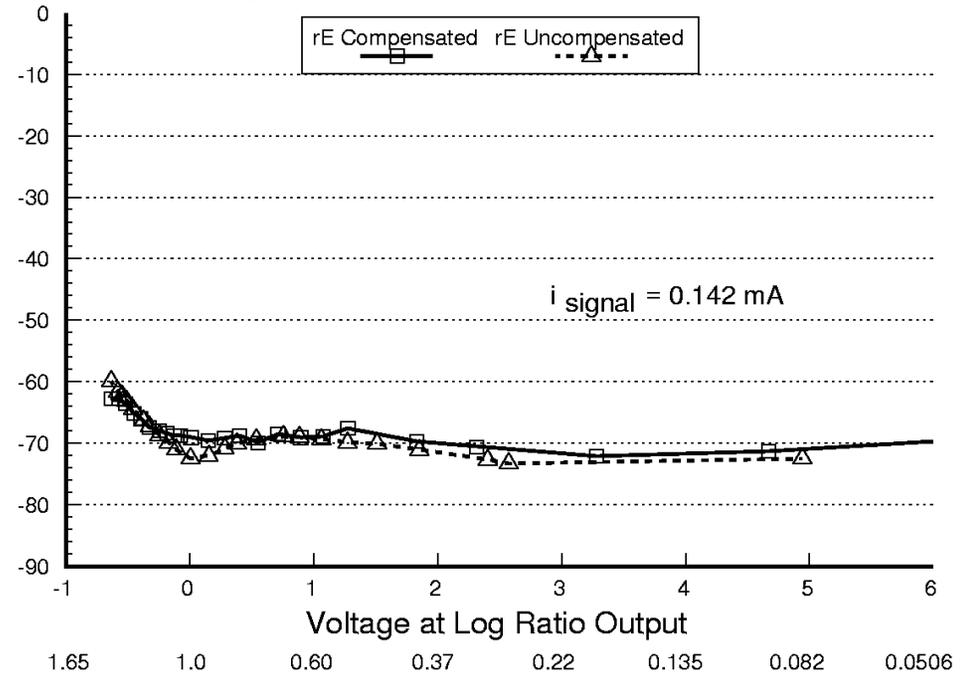

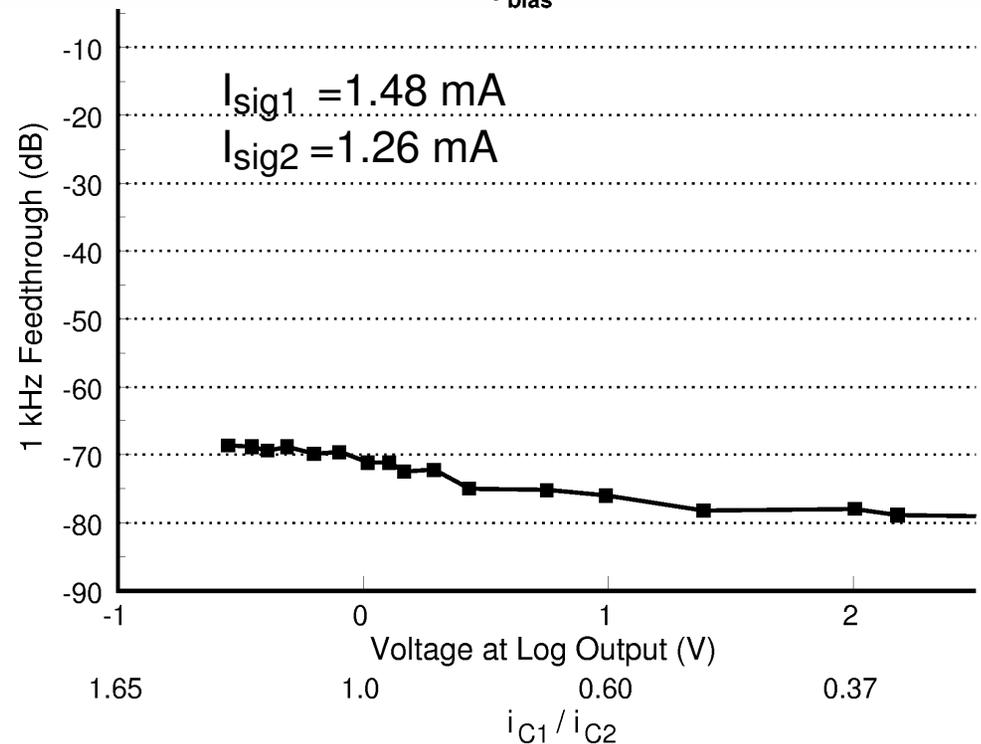
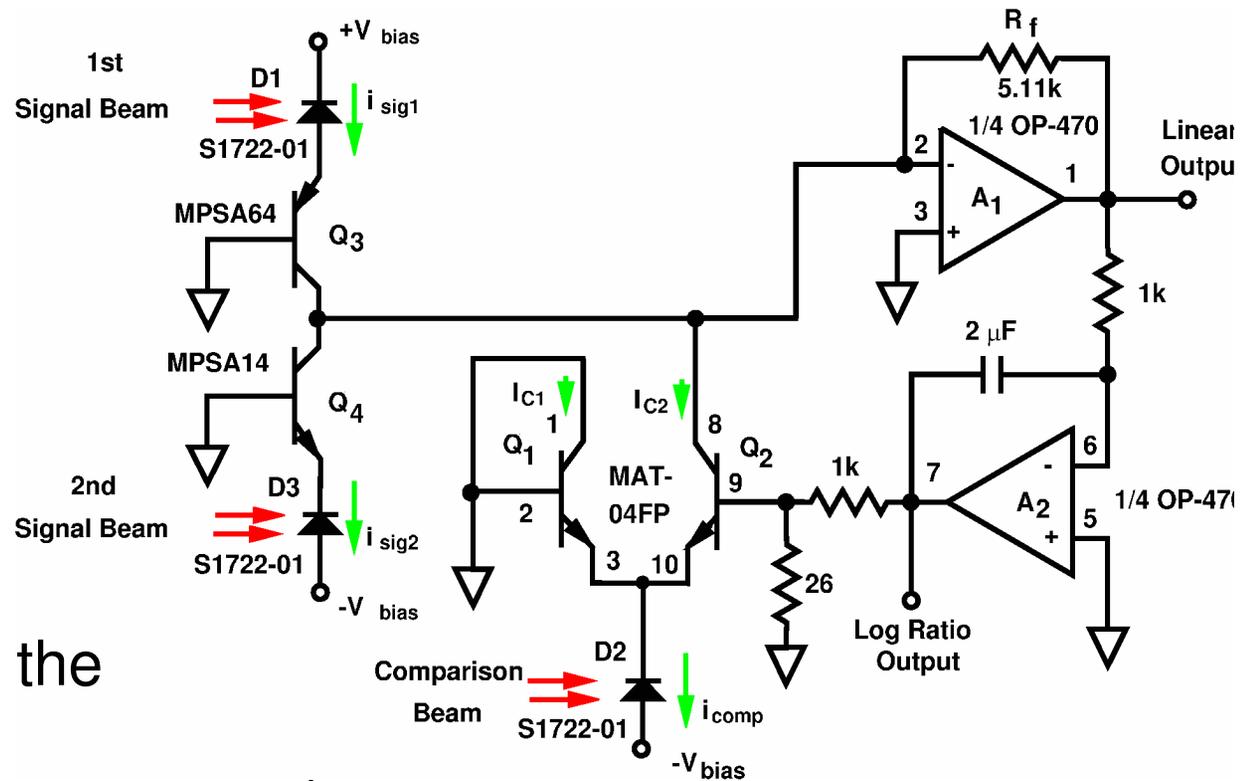
# Differential Version

- Add second signal beam
- Run slightly unbalanced ( $I_{sig1} > I_{sig2}$ )
- Differential pair sees only the slight imbalance  
 $I_{comp} > (I_{sig1} - I_{sig2}) \ll I_{sig1}$
- Limitations of BJTs circumvented
- 3 dB noise improvement (both signal beams contain information)
- Using log output requires more thought
- 160 dB SNR (1 Hz)



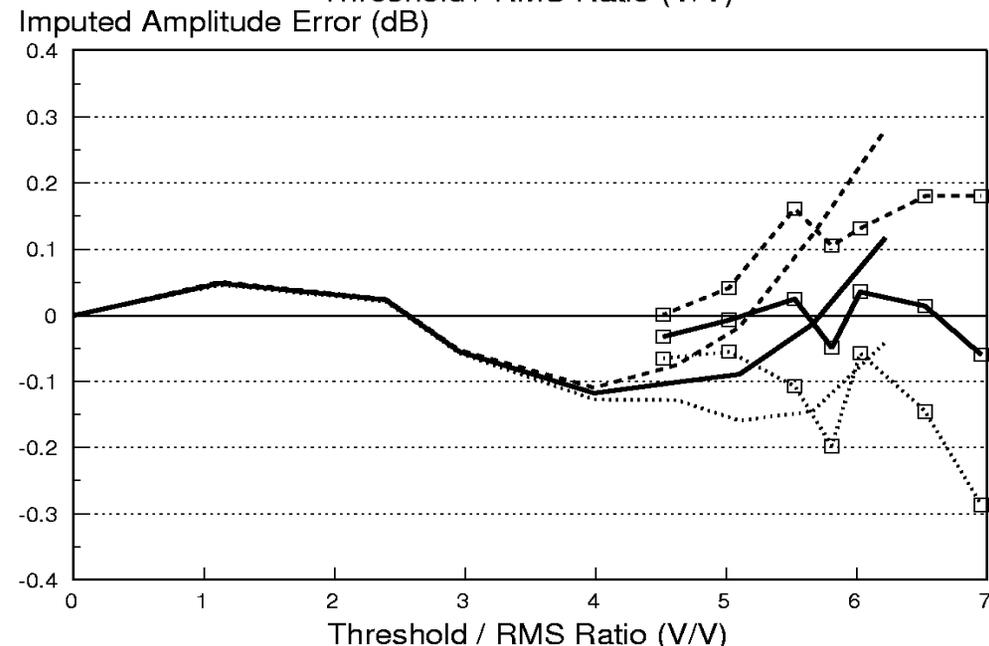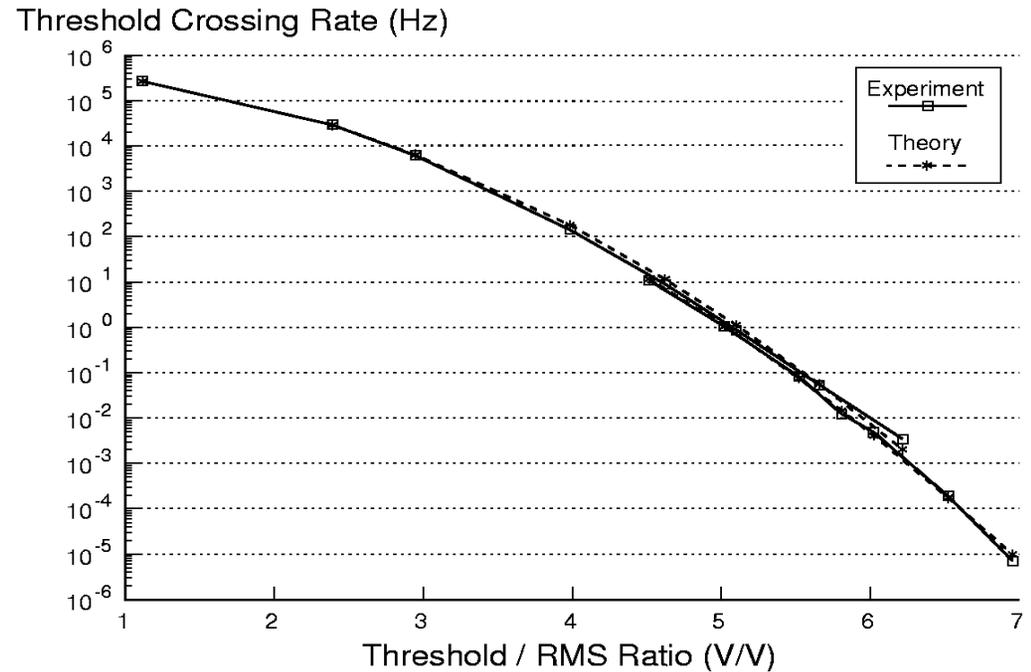
# Shot Noise False Alarm Rate

- Differential noise canceller, diode laser,  $\sim 0.5$  mW/beam
- BW = 1.1 MHz
- Beam scanning around inside a chamber with a sandblasted aluminum back wall (some mode hopping)
- Noise canceller leaves only shot noise
- Very gaussian over  $>10$  orders (300 kHz - 8  $\mu$ Hz)
- Imputed error  $\sim 0.1$  dB over full range (1-parameter fit to exact noise BW)


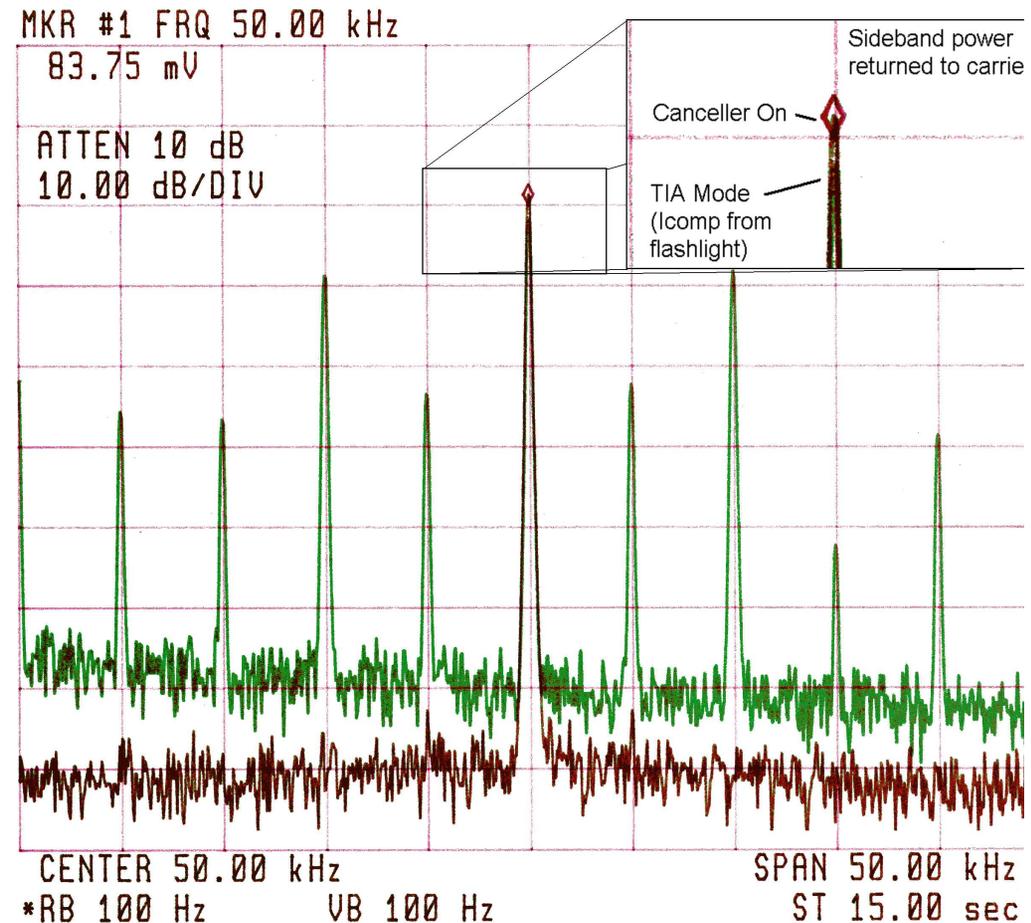
# Multiplicative Noise


- Signal beam: 50 kHz AM
- Comparison beam vs flashlight
- Laser: Distorted 30% AM at 5 kHz
- Noise intermod suppression:  
≥ 70 dB
- Power returned to signal
- Peak heights are independent of power level
- Intermod suppression depends on loop gain, but:
- The signal being ratioed has had its additive noise cancelled at all frequencies
  - ▶ Noise performance greatly improved--no additive noise!







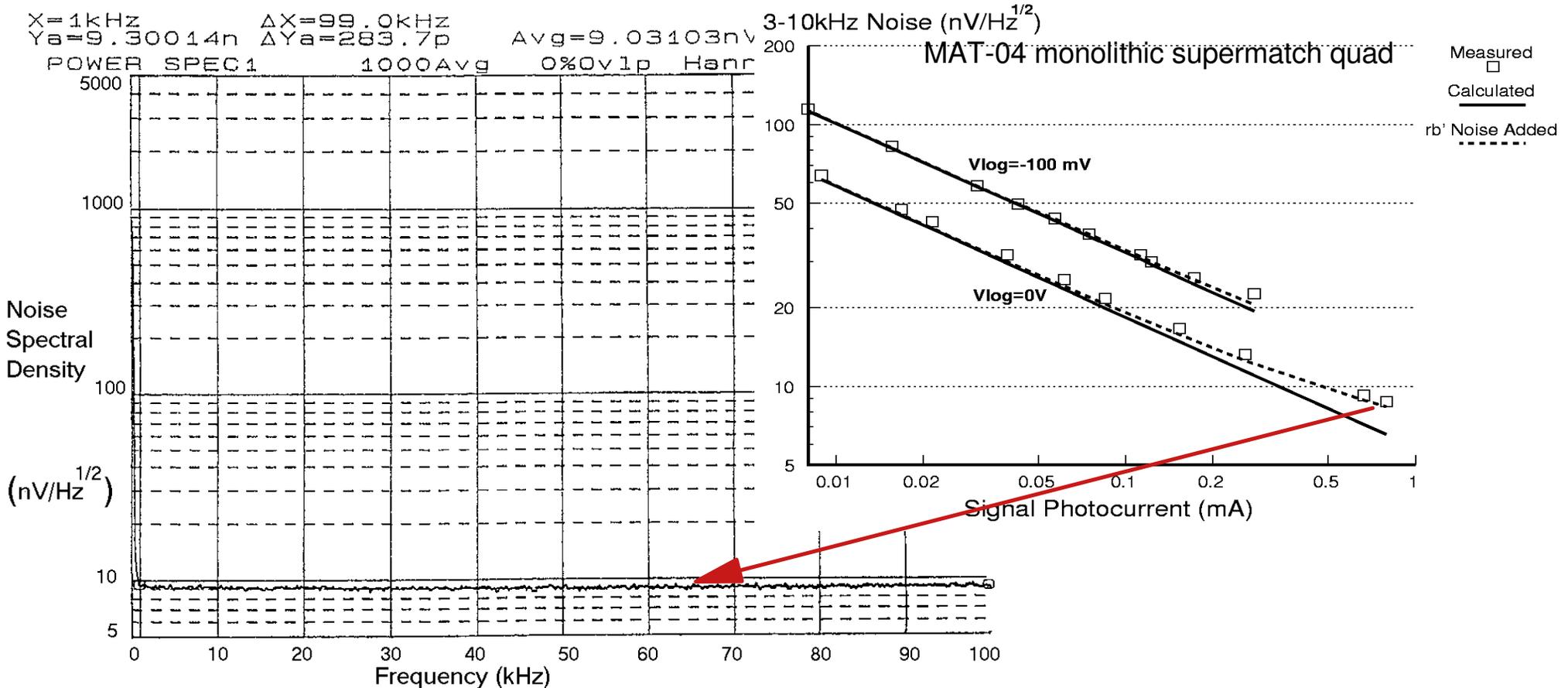
# Performance: Log Noise Floor

- Shot noise of  $I_{sig}$  and  $I_{comp}$  add in power => noise floor at least 3 dB above shot noise (but stay tuned)
- Noise floor is very flat and stable, generally within 0.5 dB of SNL except at high currents (and parallelling transistors can improve that)


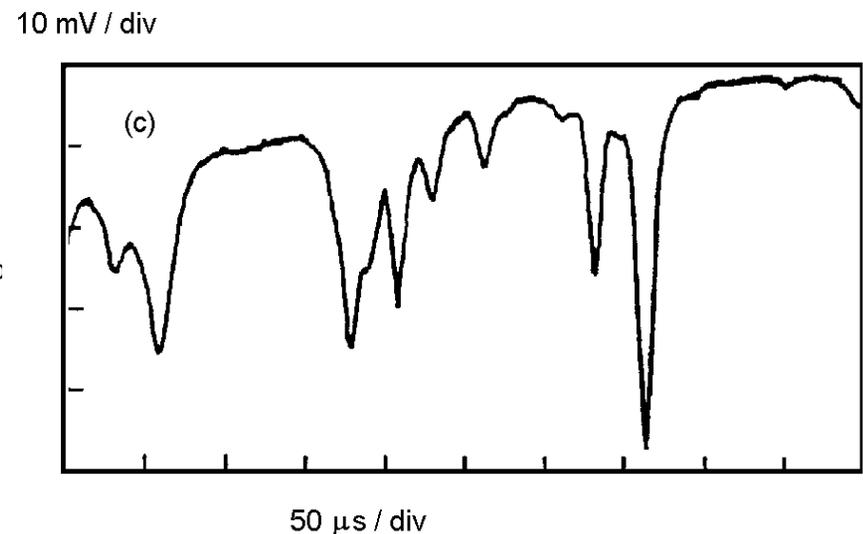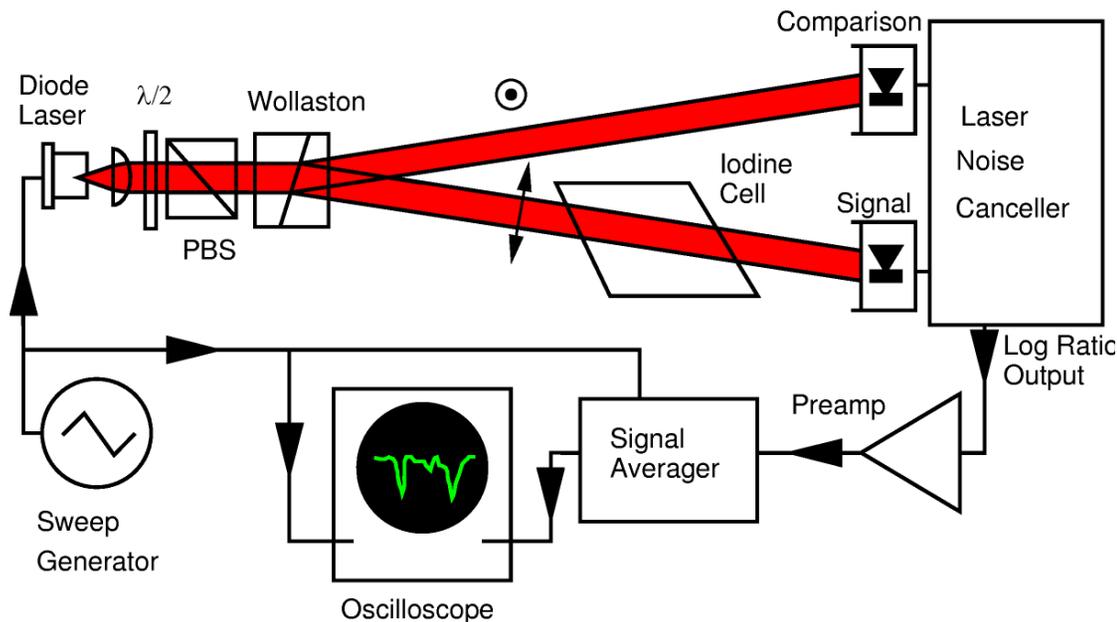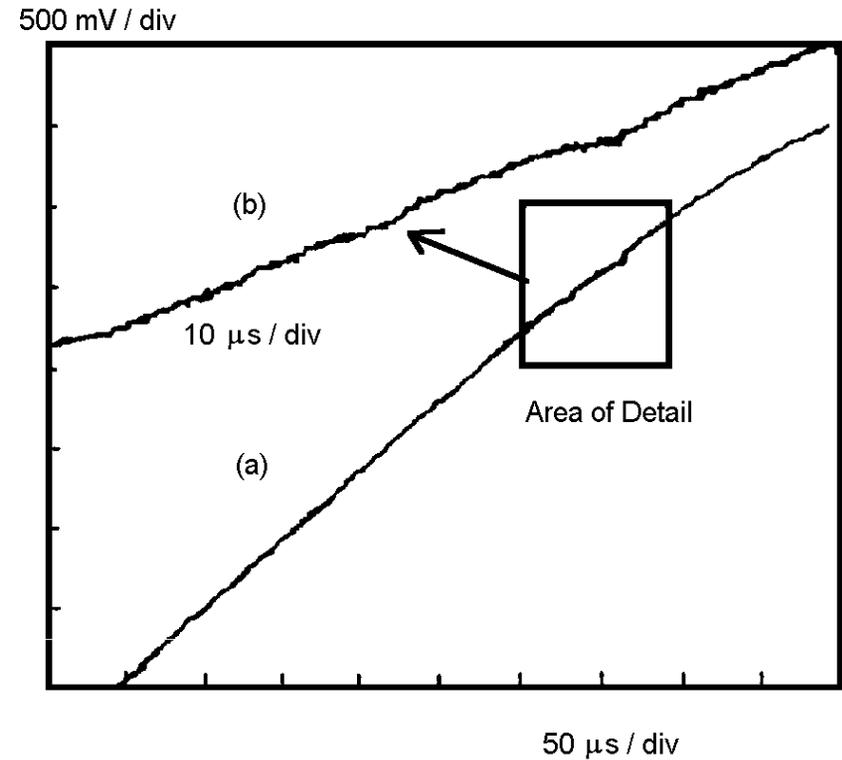
# Log Ratio Spectroscopy

- Sensitivity  $\sim 1$  ppm absorption
- Shot noise limited even with huge  $dP/d\omega$  ( $\Delta P \sim 30\%$  over scan range)
- Etalon fringes eliminated by subtracting pressure-broadened scan



# Noise Cancellers and You

- The Good News:  
A noise canceller will cancel all correlated modulation down to the shot noise level
  - ▶ Laser RIN is substantially eliminated
  - ▶ Error in ratiometric measurements is greatly reduced
- The Bad News:  
Everything else will be left behind
- Everything depends on the correlation between signal and comparison beam remaining high
- You're going to learn things about your beams that you never wanted to know: Coherence fluctuations, spatial side modes, amplified spontaneous emission, polarization instability, vignetting, and especially **etalon fringes**

# Applications Advice

## System design

- **Etalon fringes:**
  - ▶ Keep design simple, avoid perpendicular surfaces
- **Spontaneous emission:**
  - ▶ Use an efficient polarizer right at the laser
- **Spatial decorrelation:**
  - ▶ Don't vignette anything after the beam splitter
- **Path length imbalances:**
  - ▶ Keep path lengths within  $\sim 10$  cm of each other
- **Photodiode linearity:**
  - ▶ Keep current density lowish & reverse bias highish
  - ▶ Transistor linearity:  $I_D > 1$  mA requires differential model or  $R_E$  compensation
  - ▶ Keep balance somewhere near 0 V (big negative voltages hurt)

# Applications Advice

## System design

- **Temperature stability**
  - ▶ Etalon fringes drift like crazy (>10% transmission change/K)
    - Photodiode windows a common culprit
  - ▶ Log ratio output proportional to  $T_J$ 
    - Temperature-stabilize  $T_J$  using monolithic quad (MAT-04)
      - 1 heater, 1 thermometer, 2 for diff pair
      - $\sim 10^{-5}$  absorption stability in 1 hour
- **Care and feeding of photoelectrons:**
  - ▶ Never put photodiodes on cables--put the amplifier right there
  - ▶ Photodiode electrical shielding often required
- **Alarm conditions:**
  - ▶ Use a window comparator on the log ratio output to check for fault conditions, e.g. no light

# Applications Advice

## Setup & Testing

- Shot noise is easy to verify & you get the frequency response free!
  - ▶ A flashlight generates a photocurrent with exactly full shot noise
  - ▶ A dc-measuring DVM is all you need to know  $i_{N\text{shot}}$
  - ▶ Source is white => Output Noise PSD == frequency response
- Check cancellation behaviour
  - ▶ Block comparison beam to turn canceller into an ordinary TIA
  - ▶ Use a flashlight to replace  $I_{\text{comp}}$  in log ratio mode ( $\Delta V_{\text{be}}$  constant)
  - ▶ Compare  $I_{\text{comp}}$  and  $I_{\text{sig}}$  to  $\Delta V_{\text{be}}$  formula--do they agree?
- Wiggle and poke things
  - ▶ Tapping components with the eraser end of a pencil will tell you which ones are generating the fringes

# Measurement Physics

- Laser noise depends on polarization, position, and time
  - ▶ Noise is spatially variable (interference with spontaneous emission and weak spatial side modes):
    - Vignetting can destroy correlation
- Etalon fringes demodulate everything
  - ▶ Mode partition noise, FM noise, weak longitudinal side modes, and coherence fluctuations turn into AM
  - ▶ Polarizing cube has 2-5% p-p fringes if perpendicular to beam
    - FSR is only  $0.13 \text{ cm}^{-1}$  (fringes really demodulate everything)
  - ▶ Be paranoid about fringes
- Spontaneous emission
  - ▶ Has different noise than laser light & will split differently

# Measurement Physics

## ■ Coherence fluctuations

- ▶ All optical systems are interferometers

$$I_{dc} \propto \underbrace{\left( |\psi_1|^2 + |\psi_2|^2 \right)}_{\text{DC}} + \underbrace{2 \operatorname{Re} \left\{ \psi_1 \psi_2^* \right\}}_{\text{Interference}}$$

- ▶ Interferometer path imbalance of 1% of coherence length  
=> 40 dB SNR in  $\Delta\nu$ , maximum ( $|\psi_1| = |\psi_2|$ )
- ▶ Outside coherence length, fringes turn into *noise*
- ▶ Full interference term becomes noise in bandwidth  $\sim \Delta\nu$
- ▶ **Can easily dominate all other noise sources if  $\Delta\nu$  isn't  $\gg \gg$  BW**


## ■ Time delays

- ▶ Delaying one arm reduces noise correlation due to phase shift
  - To get 40 dB cancellation, phase shift  $\omega\Delta t < 0.01$  rad

# Summary: Low Frequency Front Ends

- It isn't just about detectors
- Good analogue design can give huge performance gains
  - ▶ bootstrapping
  - ▶ cascode TIAs
- Careful system design prevents trouble:
  - ▶ Etalon fringe elimination
  - ▶ Believing your noise budget
- Linear combinations--used intelligently--make hard things easier
  - ▶ Differential detection
  - ▶ Laser noise canceller
  - ▶ Cavity locking


# Footprints: Concept

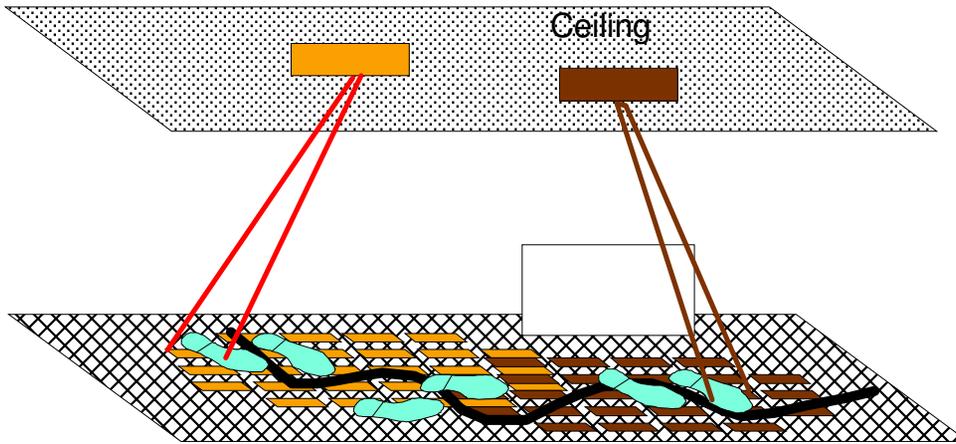

What Are My Customers Really Doing?

- Quantitative Evaluation of Store Design
- See Where Customers Go & What They Look At
- Real-time Feedback On Store Ops  
(To make it worth instrumenting every store)
  
- Distribute Cheap Sensors In The Ceiling
- Extract Trajectories Automatically


# \$10 Pyroelectric Camera

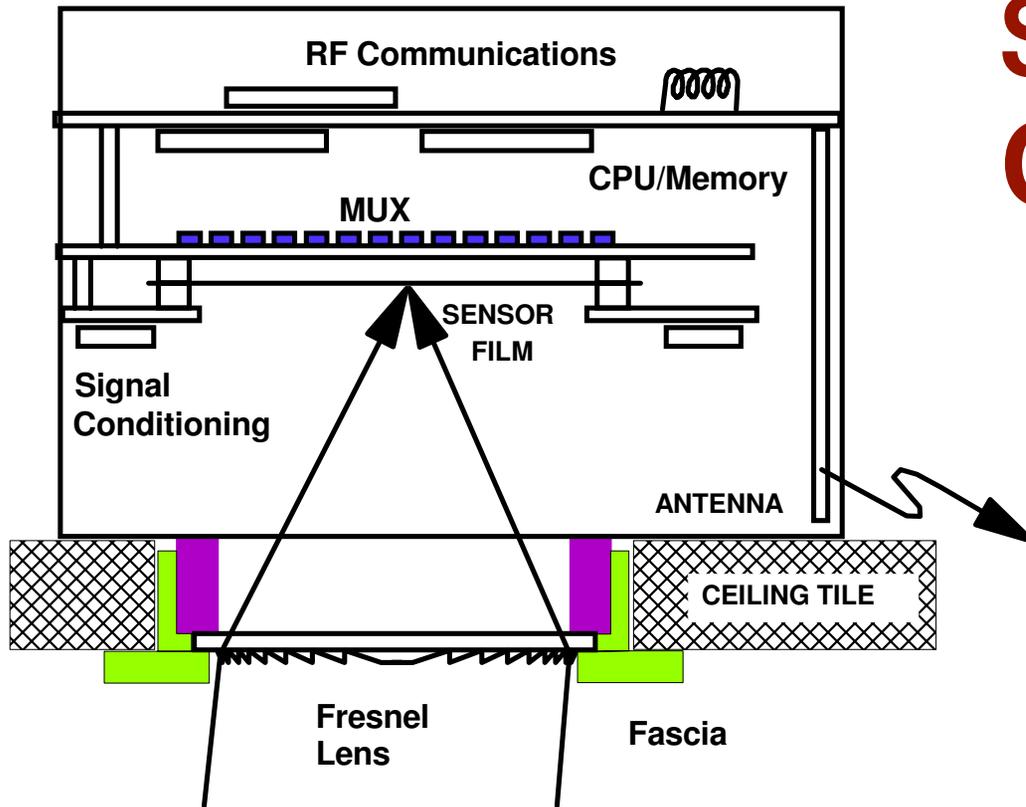

## Array of Distributed Pyroelectric Sensors


- Sensors Mounted In Ceiling
  - ~ 100 pixels/sensor
- 100-1000 Sensors Per Store (100-200 sq ft each)
- Base Manufacturing Cost: \$50-100

# Pyroelectric Effect

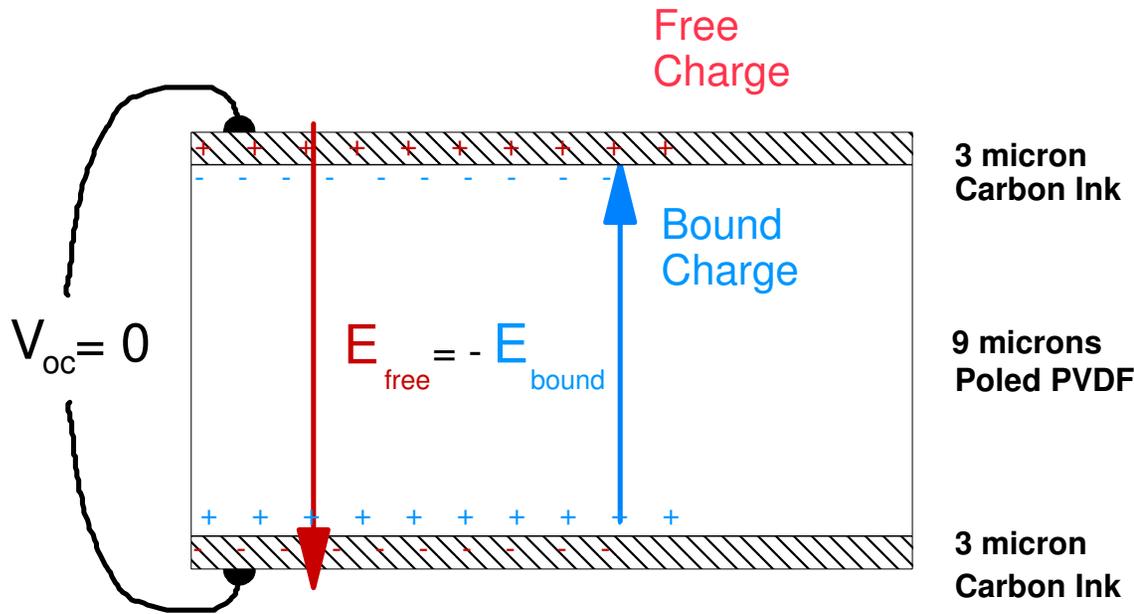

- Ferroelectric PVDF (fluorinated Saran Wrap)
- Ferroelectric Has Frozen-In  $\mathbf{E}$   
Like Remanent  $\mathbf{B}$  In A Ferromagnet
- Polarization drops  $\sim 1\% / K$
- Free Charge  $q$  Flows To Zero Out  $\mathbf{E}_{total}$ , so  $\Delta q$  gives  $\Delta T$
- Very inexpensive
- Inherently AC: Static Objects Disappear

# Multiplexed Pyroelectric Array

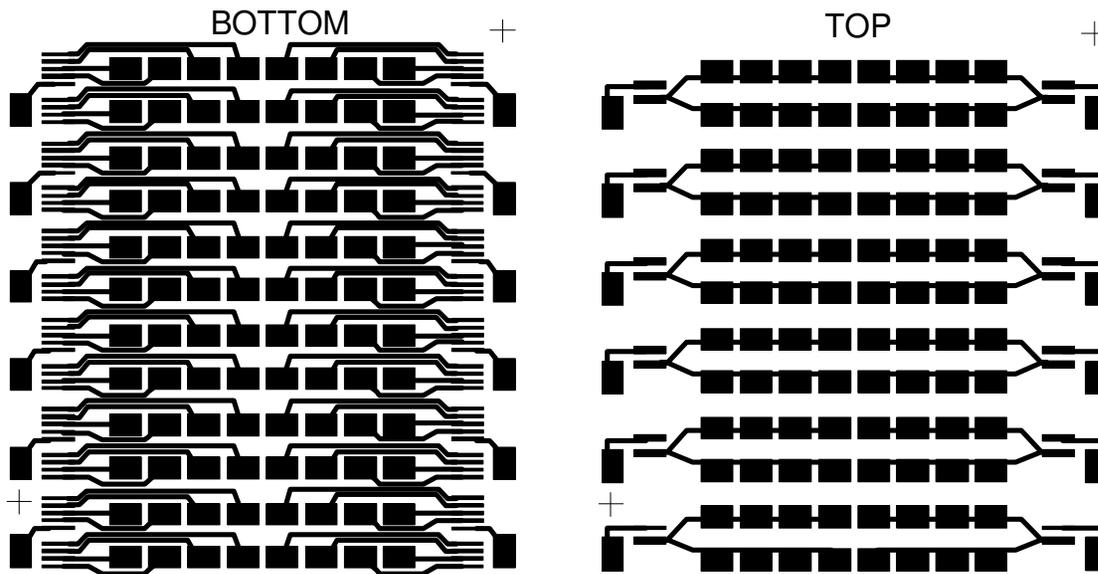

Footprints IR Sensor Photomask Rev C: POSITIVE TONE


Phil Hobbs, June 25, 1999

## IR FPA sensitivity, porch-light cost

- Free-Standing PVDF Film In Air
- 8 x 12 Array, 6 mm Pitch  
(Tee-shirt Lithography)
- Needs Fancy Multiplexer

# Optical Design



## Moulded Polyethylene Fresnel Lenses

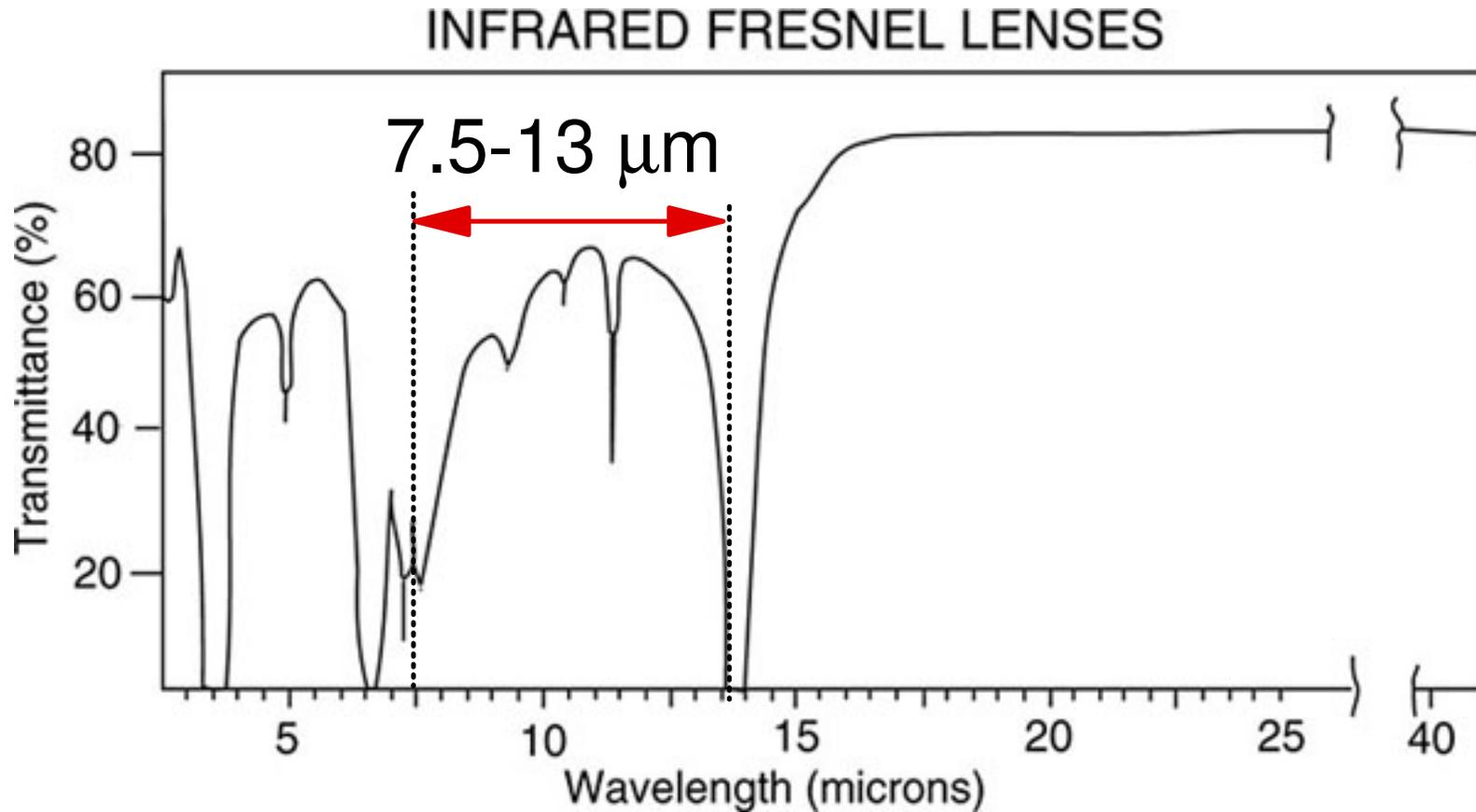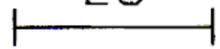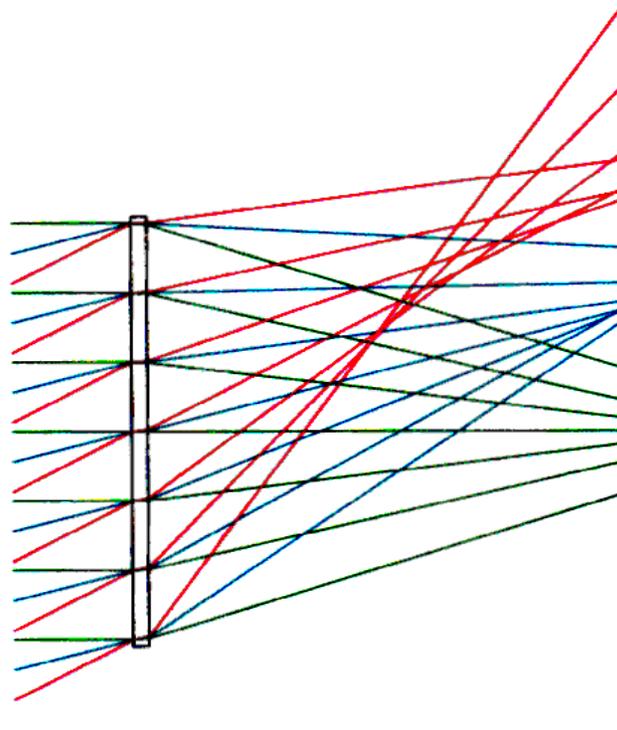

IRstart1  
OPTICAL SYSTEM LAYOUT

UNITS: MM  
DES: Budd


25

A horizontal scale bar with vertical end caps, indicating a length of 25 units.

# Thermal Design
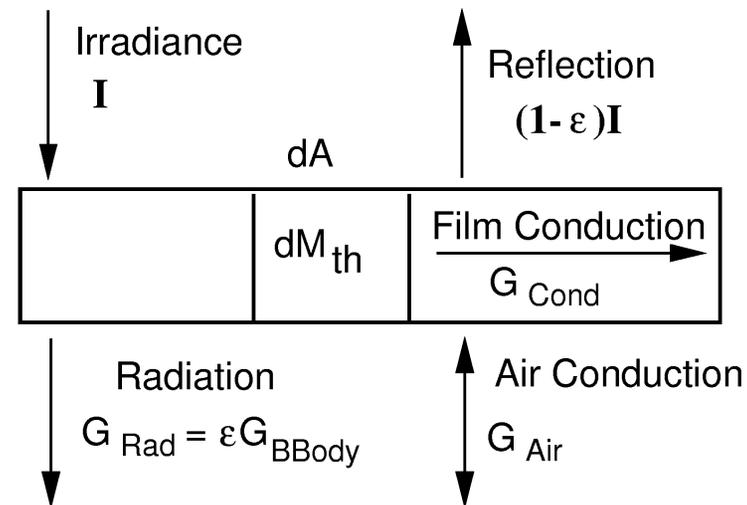
## Slow is Beautiful


- Signal Power  $\sim G^{-2}$
  - Johnson Noise Is Flat
  - (Fluctuation PSD  $\sim G$ )
  - Bandwidth  $\sim G/M_{th}$
  - Johnson-Limited SNR  $\sim 1/G$
- => Insulate the Sensor & Filter Data To Recover BW




$$G_{Total} = G_{Rad} + G_{Cond} + G_{Air}$$

$$\Delta T = \epsilon I / G_{Total}$$

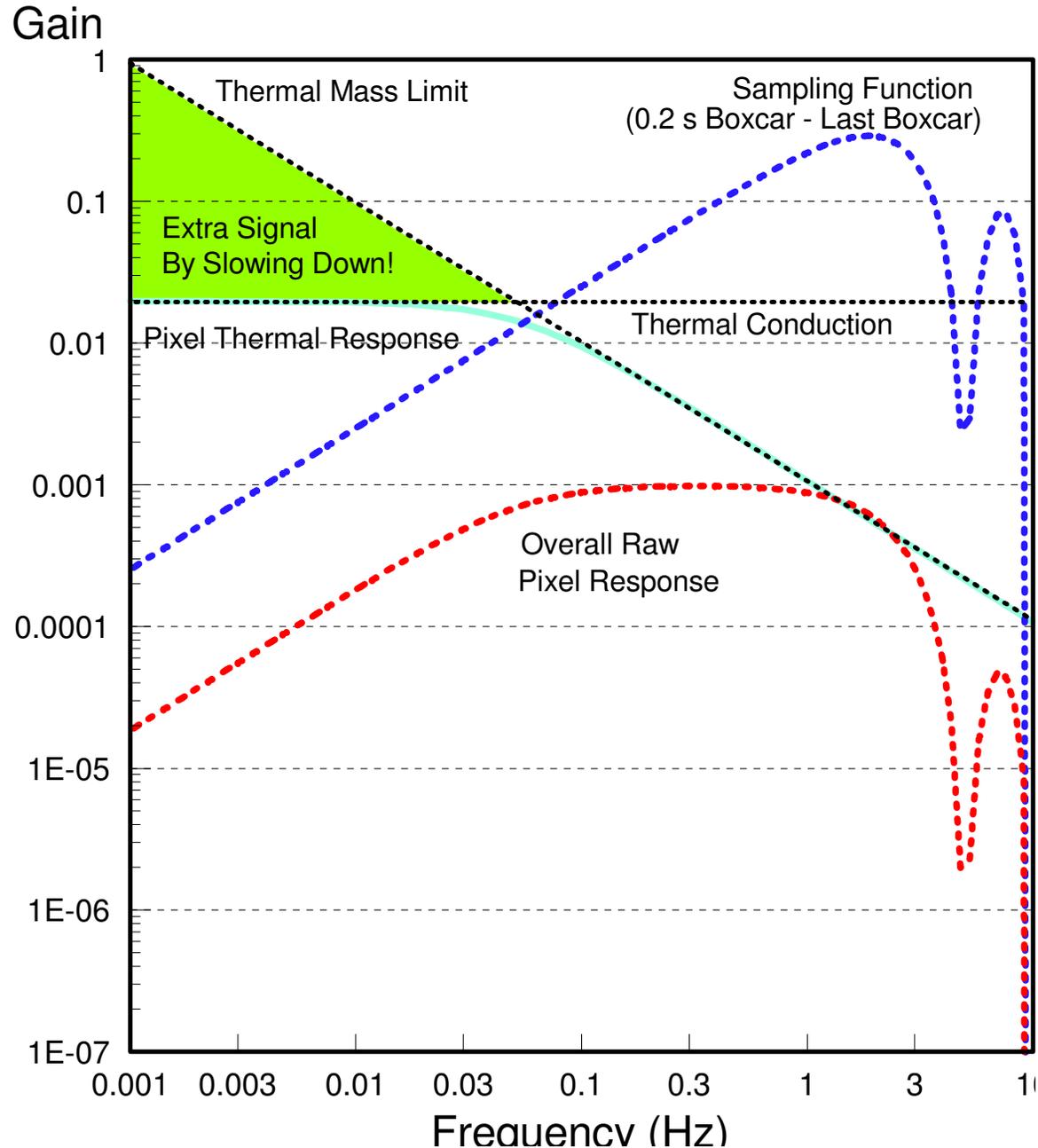
$$dT/dt = (\epsilon I - G_{Total} \Delta T) / (dM_{th} / dA)$$



# Thermodynamic Efficiency

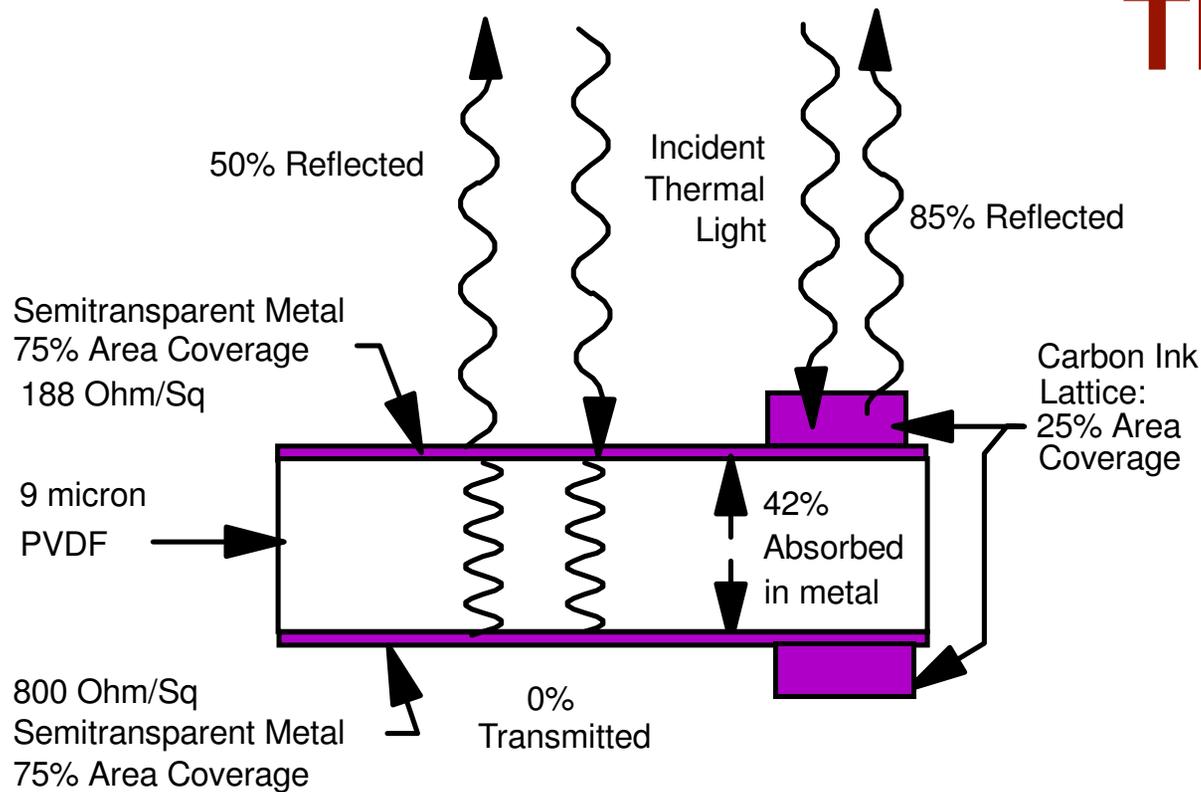

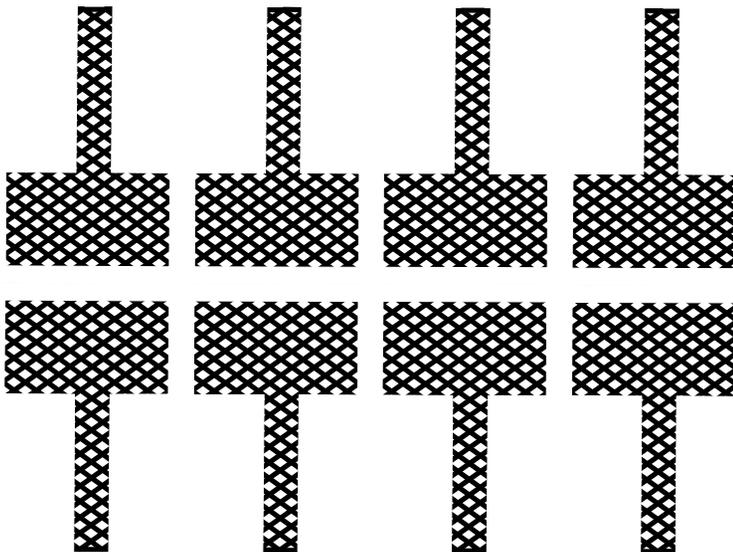- Sensitivity proportional to surface emissivity
- Carbon ink is shiny at  $10\ \mu\text{m}$
- "Swiss-cheese" ink blanket halves the thermal mass
- Tuned metal coating increases  $\Delta T$
- Ink lattice on tuned metal should give  $\sim 20\ \text{dB}$  more signal



# Sensor Design: Multiplexer

- $\Delta T_{\text{pixel}} \sim 8 \text{ K}$  (Human Crossing the Floor)
- $\Delta q / \Delta T_{\text{pixel}} = (3\text{V/K})(160 \text{ pF}) \sim 500 \text{ pC/K}$   
BUT:  $\Delta T_{\text{pixel}} / \Delta T_{\text{IFOV}} \sim 0.002$ ,  $\tau \sim 2 \text{ s}$  (10 Frames)  
Total Signal Available  $\sim 0.1 \text{ pC/pixel/frame}$
- Multiplexer Leakage  $\leq 5 \text{ pA}$
- Charge Injection  $< 0.5 \text{ pC}$
- Nothing like it is available commercially

# Diode Switches


- Nanoamp Leakage
- Control And Data Paths Not Separate
- **Unidirectional And Nonlinear: Bias Required**

$$I_F = I_S \left( \exp\left(\frac{eV_f}{kT}\right) - 1 \right) \quad R_0 = \left. \frac{\partial V_F}{\partial I_F} \right|_{V_F=0} = \frac{kT}{eI_S}$$

- 1 mA  $I_F$ : Si diode  $\sim 0.65$  V, LED  $\sim 1.6$  V  
 $\Rightarrow I_S$  for a LED Should Be  $10^{-16}$  That of Si
- \$0.05 LED has  $|I_F| < 100$  fA,  $-5$  V  $< V_F < +0.5$  V

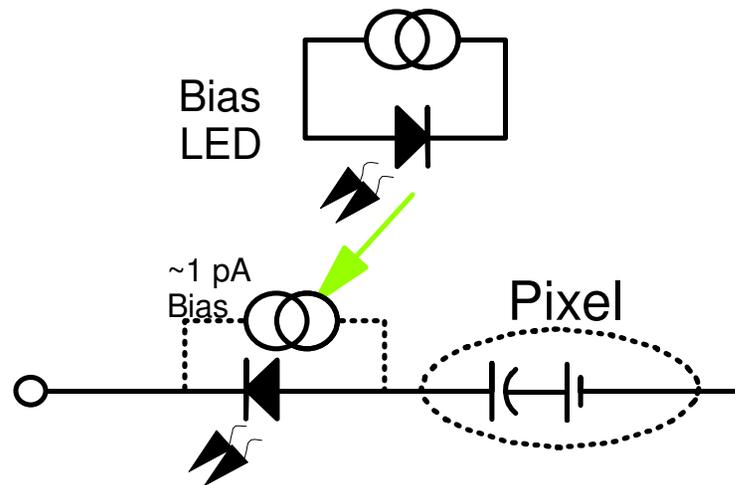
# Biasing Hack

- Need 1-5 pA Bias Per Pixel, CPU Adjustable
- $10^{12} \Omega$  Resistors Don't Come in SMT
- **Use Photocurrent Instead**




- LED Is a Photodiode Too
- Use **Diffused Light From CPU-Throttled LEDS**
- **1 mA LED Drive => 1 pA Bias**
- **Switch + Adjustable Bias = 1 LED @ \$0.05/Pixel**


# LED Mux Schematic

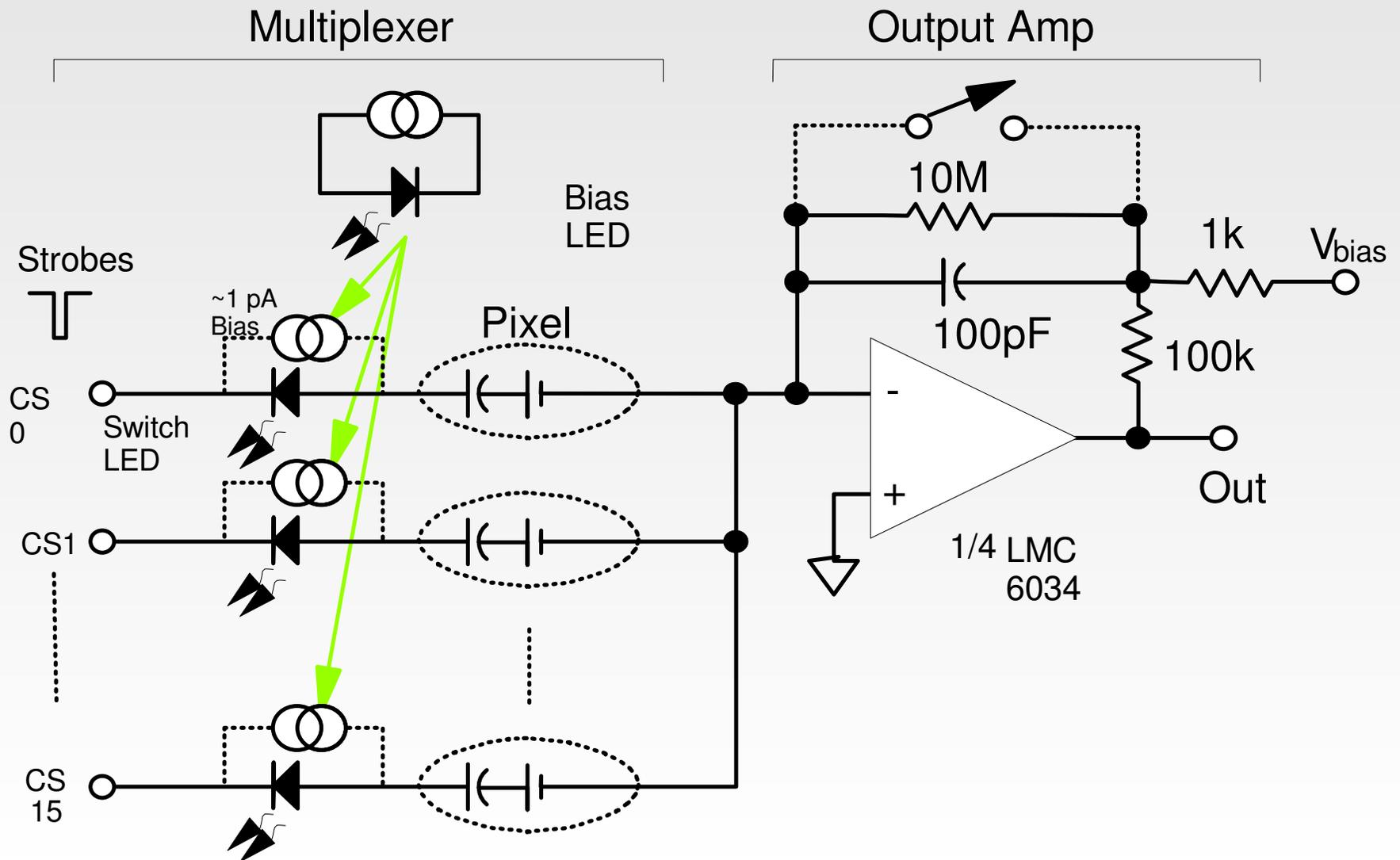

# Footprints Data

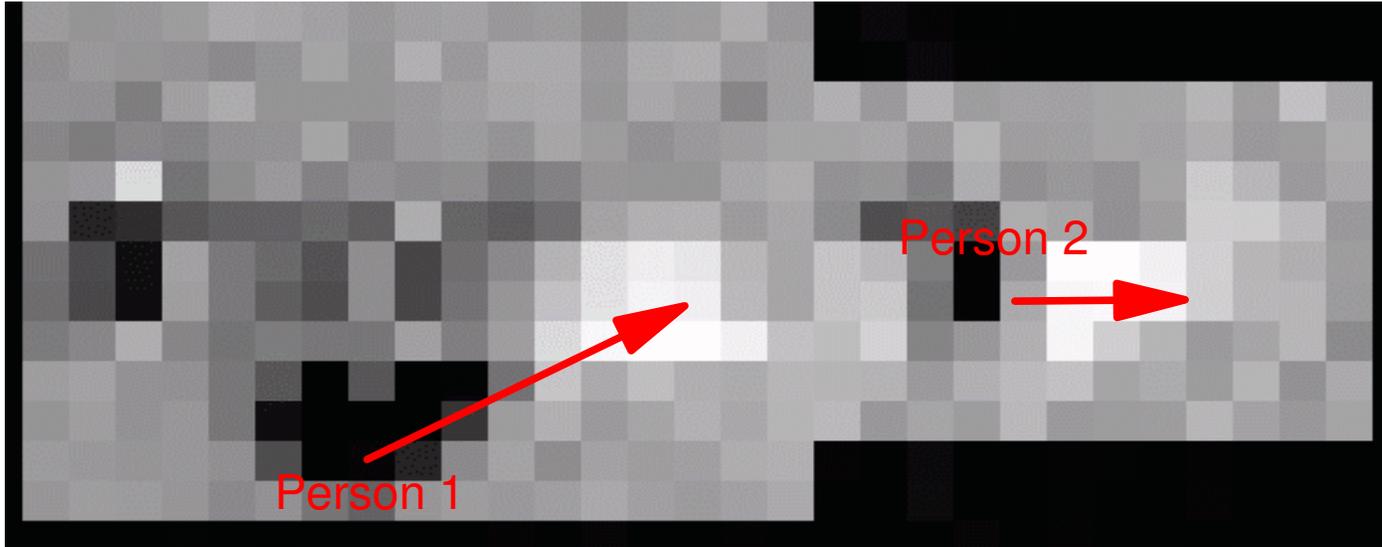


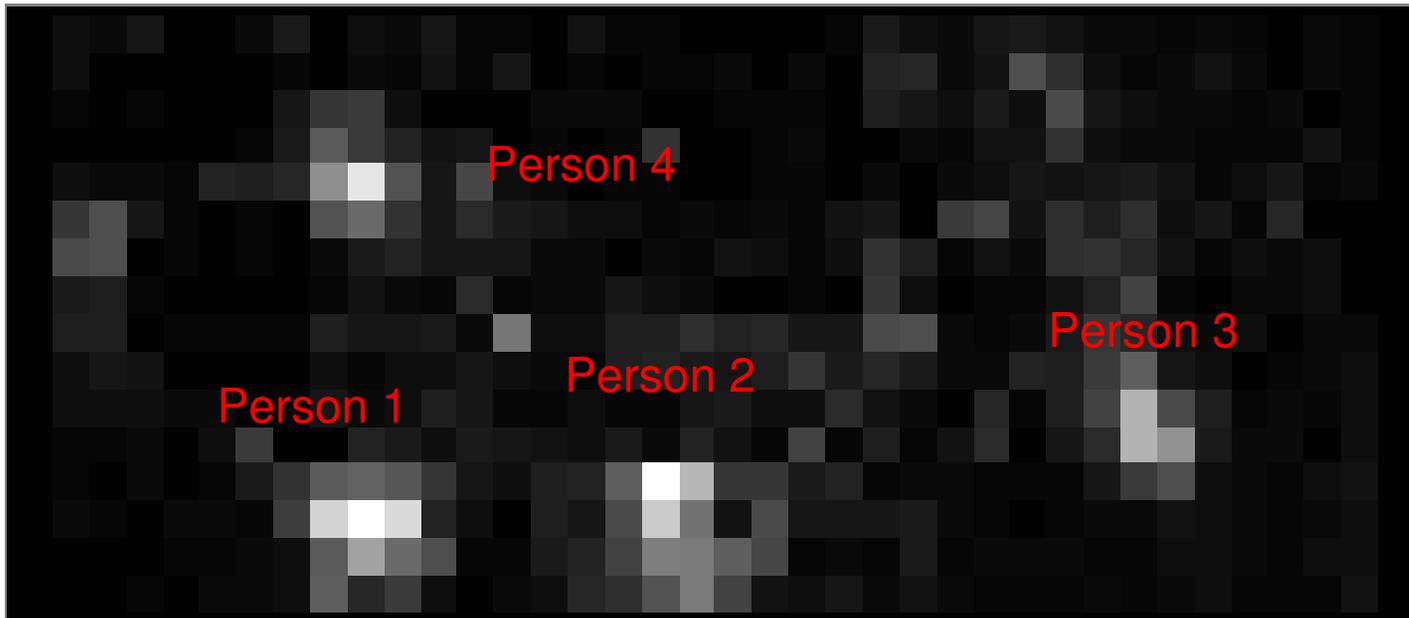(Raw data,  
1 sq ft pixels,  
28  $\mu\text{m}$  metallized  
PVDF)



(Pseudo-integral,  
1 sq ft pixels, 4  $\mu\text{m}$   
carbon ink on 9  $\mu\text{m}$   
PVDF)

# Footprints Data

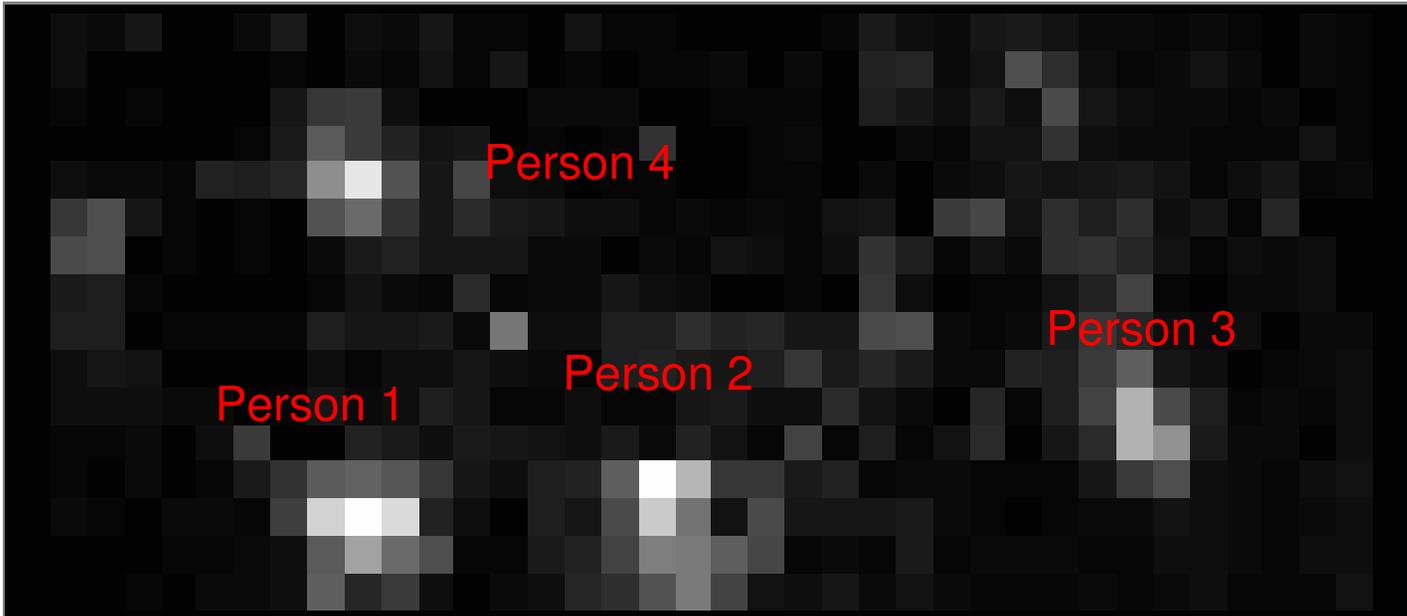

(Pseudo-integral,  
1 sq ft pixels, 4  $\mu\text{m}$   
carbon ink on 9  $\mu\text{m}$   
PVDF)

**More if time permits....**

# Going Faster: RF Techniques

- TC reduction goes only so far
  - ▶ Impedance Transformation
  - ▶ Reactive networks
  - ▶ Transmission-line transformers
  - ▶ Constant-resistance T-coils
- Low-noise RF amps
  - ▶ 35K noise temperature: 9 dB improvement vs 300K
  - ▶ Driving 50 $\Omega$

# Noise Figure & Noise Temperature

- Ways of quoting low noise levels
- Noise Figure
  - ▶  $NF = 10 \log[(SNR \text{ before})/(SNR \text{ after})]$  (300K source)
  - ▶ 3 dB is garden-variety
  - ▶  $< 0.4$  dB is the state-of-the-art @ 1-2 GHz (Miteq)
- Noise Temperature
  - ▶ Very low NFs awkward to use
  - ▶  $T_N = P_N / (kB)$
  - ▶  $T_N = 300K(10^{NF/10} - 1)$
  - ▶ 3 dB NF = 300K  $T_N$ , 0.5 dB NF = 35K  $T_N$ , LT1028 = 15K (@1kHz)
  - ▶  $T_N \ll T_{\text{ambient}}$ ! (F-D theorem doesn't apply to active circuits--or refrigerators for that matter)

# Impedance Transformation

- PD is a current source
  - ▶ Signal power proportional to  $\text{Re}\{Z_L\}$
  - ▶ Increasing  $Z_L$  at the diode can improve SNR
  - ▶ Want all-reactive networks
    - Resistors in the matching network dissipate power uselessly and add a 300 K noise source to a  $\sim 40$  K system
- *Not an impedance matching problem for  $\lambda < 1.8 \mu\text{m}$ !*
  - ▶ Available power not fixed for Si, InGaAs PDs
  - ▶ Source impedance poorly defined
  - ▶ IR diodes, e.g. InAs, InSb, HgCdTe have low shunt resistances:
    - Available power is fixed, so impedance matching is relevant

# Impedance Transformation

## ■ Low Noise Amps

- ▶ PD is a nearly-pure reactance => almost noiseless
- ▶ 35K amp is 9 dB quieter than 300K amp for reactive source
- ▶ BJT emitter ideally has  $T_N = T_{\text{amb}} / 2$ ,
  - ideal BJT base has  $T_N = T_{\text{amb}} / (2\beta)$ --same noise voltage,  $\beta$  times higher impedance
- ▶ Connect PD straight into MMIC with no resistor or capacitor--fix frequency funnies afterwards, at higher signal levels

## ■ Transformers

- ▶ Quiet RF amps are all around 50  $\Omega$  (amps are typically 2:1 VSWR, so it might be 100 $\Omega$  or 25 $\Omega$  )
- ▶  $N$ :1 turns ratio gives  $N^2$  impedance change
- ▶ Transform 50  $\Omega$  up for Si PD, or down for, e.g., InAs

# Bode Limit

- How wide can we go?


- ▶ Bode theorem specifies tradeoff between BW and insertion gain  $\Gamma$

$$\int_0^{\infty} \ln\left(\frac{1}{|\Gamma|^2}\right) d\omega \leq \frac{2\pi}{RC}$$

- $|\Gamma|^2$  is the return loss (fraction of power reflected from the load)
- RC has 1.03 dB average passband loss (to 3 dB points)
- Choose  $|\Gamma|^2 = 0.21$  (79% efficiency, or 1.03 dB signal loss)
  - ▶ BW increases 4x vs RC, for no net signal loss whatsoever
- 3 elements will usually get within 0.5 dB of this limit
- Increasing mismatch gains bandwidth almost reciprocally
  - ▶  $|\Gamma|^2 = 0.5$  gives 9x BW @ 3 dB loss

# L-Network or Series Peaking


## ► Simplest Reactive Network

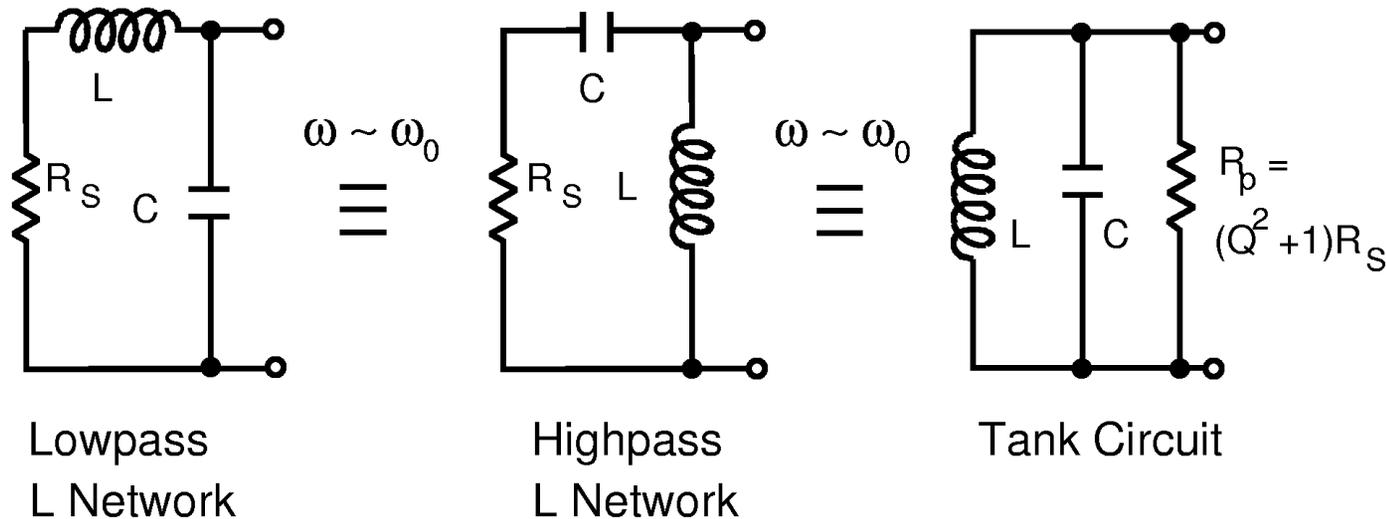

- Moves RC bandwidth from DC to  $f_0$  (same BW, settling time doubled)
  - $Q = X/R$  [at resonance,  $Q = 1/(\omega_0 RC)$  (ratio of  $f_0$  to  $f_{RC}$ )
  - Bandwidth  $BW_{3dB} = \omega_0/Q$
- **Transforms load impedance by a factor of  $Q^2 + 1$** 
  - $50 \Omega$ ,  $Q = 10 \Rightarrow$  effective RL =  $5k\Omega$  (pure resistance at  $\omega_0$ )
  - Can also be used at baseband for a 1.4x BW increase

# Constant-Resistance T-Coil

## ► Tektronix Vertical Amplifier Secret

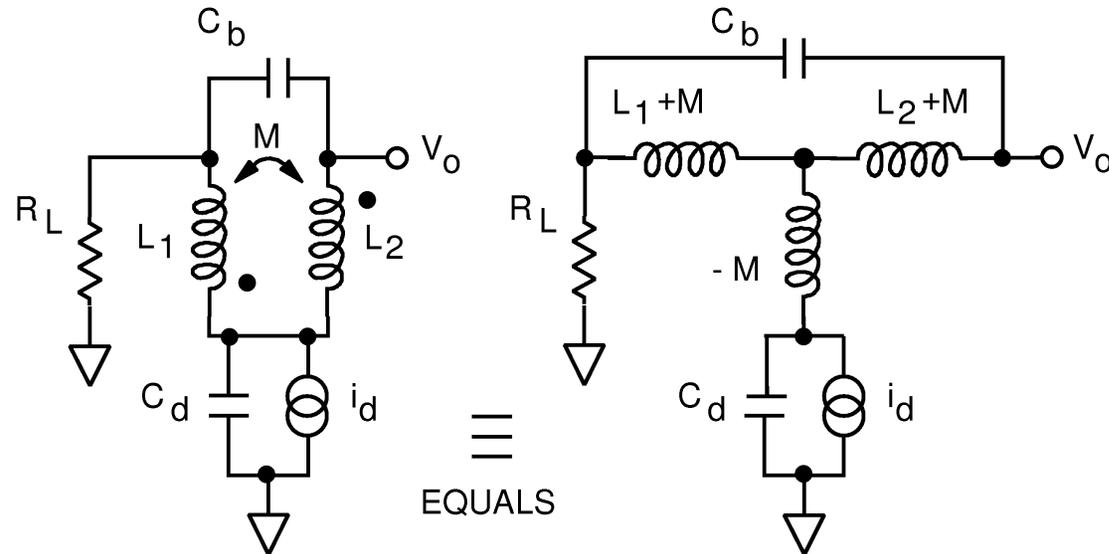


Doesn't waste current in  $R$  while there's  $C$  to charge

- 2.8x BW increase (at 3 dB points)
- No overshoot or ringing
- **Design equations available**
- Best simple network for baseband use (lowpass characteristic)
- Disadvantage: Load resistor and output are different nodes
  - Harder to get  $T_N < 300K$  (may have to put active device in for  $R$ )

# Example: 5 pF PD, DC-50 MHz

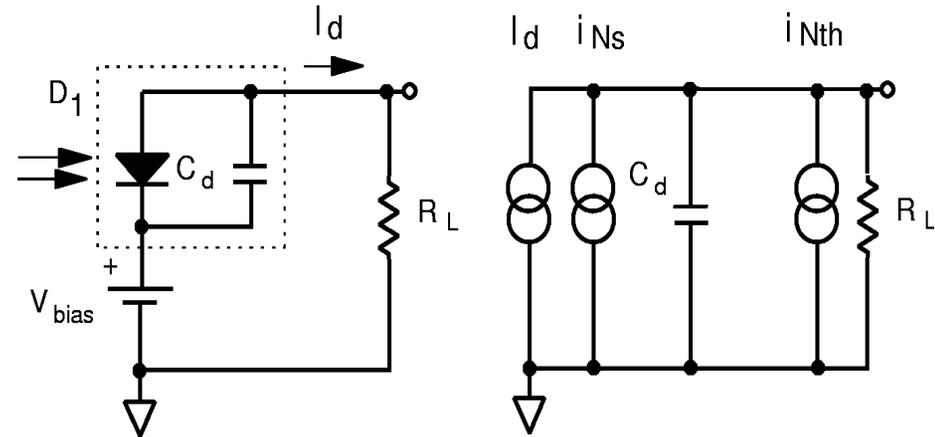
## ■ Direct connection to 50 $\Omega$

- ▶  $BW = 1/[2\pi(5\text{pF})(50\Omega)] = 640 \text{ MHz}$
- ▶ Shot noise limit:  $I_{\text{phot}} \geq 1 \text{ mA}$   
(300K),  $370 \mu\text{A}$  (35K)
- ▶ *Wasteful*


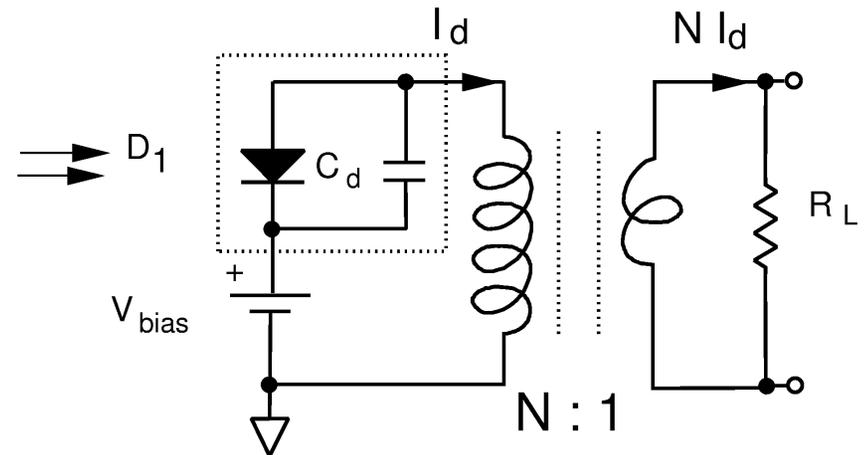
## ■ 3:1 Turns Ratio Transformer (450 $\Omega$ )


- ▶  $BW = 1/[2\pi(5\text{pF})(450\Omega)] = 70\text{MHz}$
- ▶ Shot noise limit:  $I_{\text{phot}} \geq 115 \mu\text{A}$   
(300K),  $13 \mu\text{A}$  (35K)
- ▶ (DC current x AC resistance  
> 50 mV (300K), > 6 mV (35K))
- ▶ *9 dB SNR improvement (Johnson limit)*



# Example: 5 pF PD, DC-50 MHz
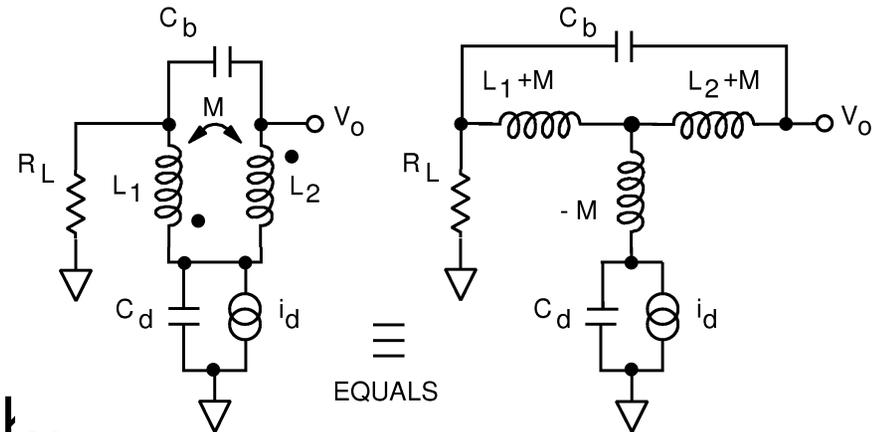
## ■ Constant-Resistance T-Coil:

- ▶ 2.8x BW increase, resistive load
- ▶ Can be used with 6:1 transformer
- ▶  $R_L = 1800\Omega$
- ▶ SN Limit: 29  $\mu\text{A}$  (300K), 3.4  $\mu\text{A}$  (35k $\nu$ ,
- ▶ Best step response
- ▶ **15 dB SNR improvement**



## ■ Bode Limit:

- ▶ 4x BW increase, resistive load
- ▶  $R_L = 2550\Omega$
- ▶ SN Limit: 20  $\mu\text{A}$  (300K), 2.4  $\mu\text{A}$  (35K)
- ▶ **17 dB SNR improvement**
- ▶ **Beyond there, you have to trade off SNR or reduce  $C_d$**

# Example: 5 pF PD, 250±5 MHz

- Put passband anywhere you like
  - ▶ Simple 81 nH series  $L$ , 5  $\Omega$  load
  - ▶  $R_L=3130 \Omega$  (Q=25--no higher)
  - ▶ Use e.g. a cascode or 1:3 xfrmr
  - ▶ Can tune by changing  $V_{bias}$
  - ▶ SN Limit: 16  $\mu\text{A}$  (300K), 2  $\mu\text{A}$  (35K)
  - ▶ 17 dB SNR improvement vs 50  $\Omega$

- Bode Limit:
  - ▶ 4x BW increase, resistive load
  - ▶  $R_L=12.8 \text{ k}\Omega$
  - ▶ SN Limit: 4  $\mu\text{A}$  (300K), 0.5  $\mu\text{A}$  (35K)
  - ▶ 24 dB SNR improvement vs 50  $\Omega$

